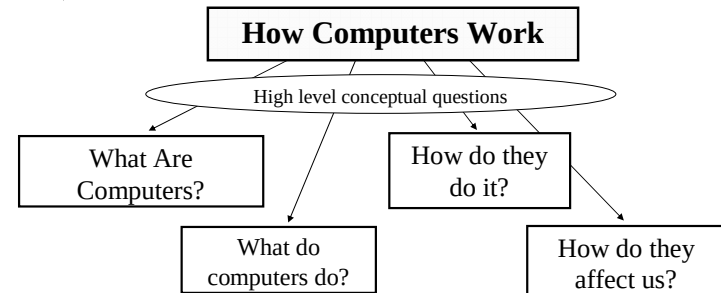


# Binary Addition


## Boolean Algebra & Logic Gates

CSC 103

September 12, 2007


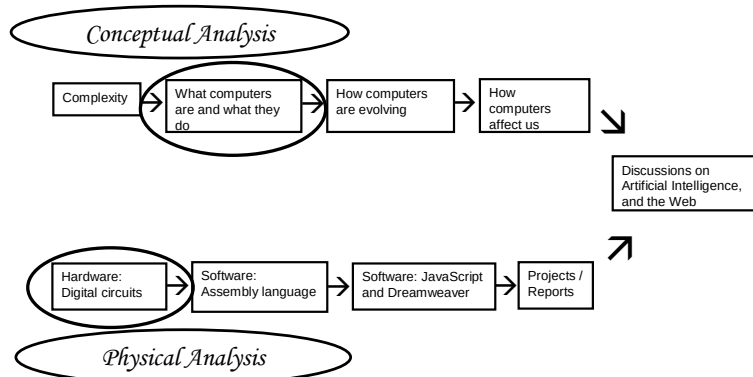
### How Computers Work: Semester Overview (Two paths for class discussions)



### Recap from Monday

- Binary numbers (§ 1.1.1)
  - The computer stores everything as binary numbers
    - Data – numbers, text, music...
    - Instructions for programming
    - Locations / addresses

## Overview for Today

---

- Binary concepts and binary numbers
- Circuit simulator
- Binary addition
  - Truth table
  - Half adder circuit


## Binary Numbers: Physical Representation

---

- Concept of “on” and “off” for physical manufacturing of computers
- Basic component
  - Switch  $\Rightarrow$  Allows control of “on” & “off”
  - Historical versions?
    - 
    -
  - Current implementation – the transistor

## Transistors

---

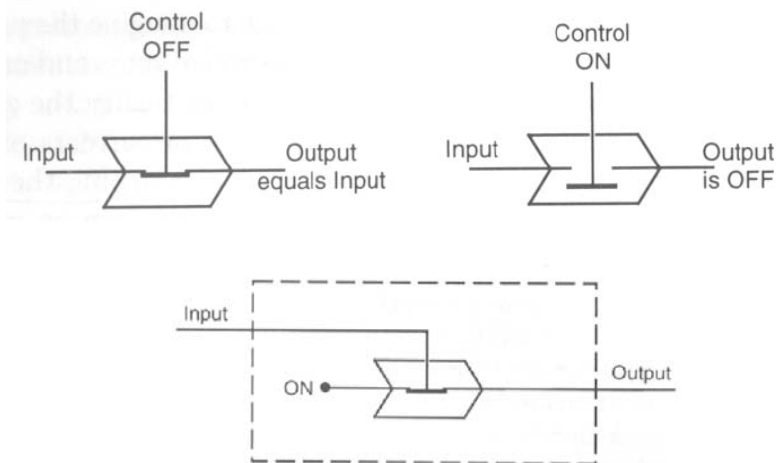

## Binary Numbers: Abstract Representation

---

- Logic
  - Provides the primary logic functions of AND, OR, NOT
- Logic gates & logic circuits
  - Symbolic representation of basic logic functions to build circuits

## Logic Functions: NOT

- One input and one output
  - Output = input *or*
  - Output  $\neq$  input
- The 'NOT' function

| A | A' |
|---|----|
| 0 | 1  |
| 1 | 0  |


## Logic Functions: AND, OR

- Two inputs, one output
- The 'AND' and 'OR' functions


| A | B | AND ( $\cdot$ ) | OR ( $+$ ) |
|---|---|-----------------|------------|
| 0 | 0 | 0               | 0          |
| 0 | 1 | 0               | 1          |
| 1 | 0 | 0               | 1          |
| 1 | 1 | 1               | 1          |

- This is a *truth table*


## Logic Gate: AND Function

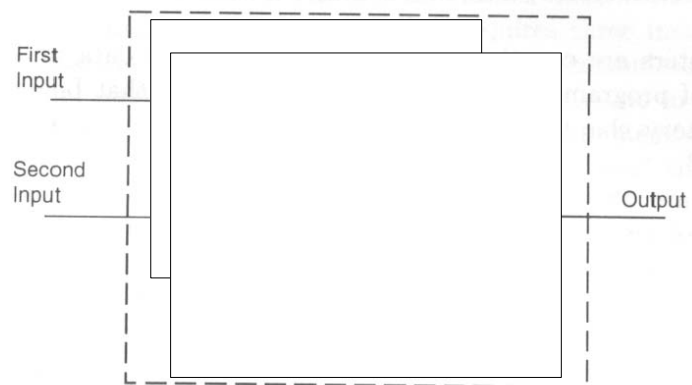

## Logic Gate: OR Function

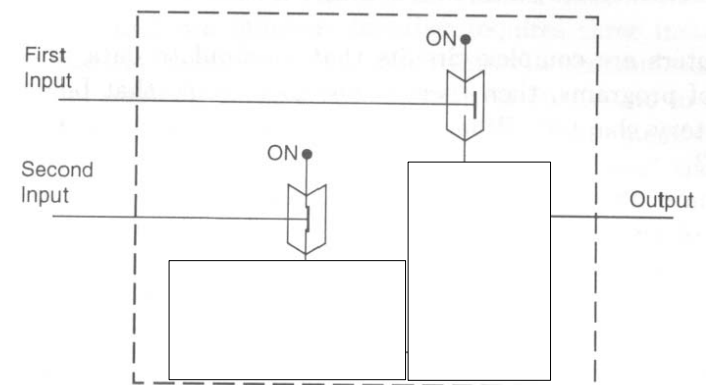

## Logic Gates: Symbols

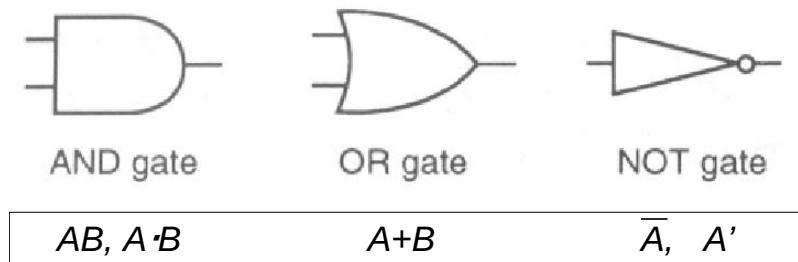


## Use of Logic Gates

- Data is represented by 1s and 0s
  - '1' means there is current or voltage
  - '0' means there is no voltage or current
- Digital circuits (*e.g.*, MP3 players, cell phones, computers)
  - These circuits are **all** constructed with AND, OR and NOT gates
- ANY** digital circuit can be built with AND, OR and NOT gates

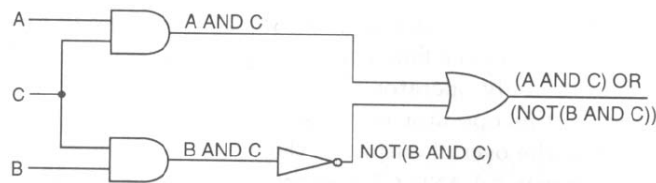
## Logic Circuit Example

- How do we implement the following function as a circuit?
  - $AC + (BC)'$
  - In words this is:
  - As a circuit this is:



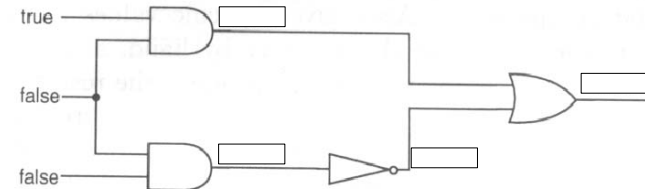
## Logic Circuit Example con't

- Implementing the following function
  - $AC + (BC)'$
  - $A = 1$  or true
  - $B = 0$  or false
  - $C = 0$  or false



## Exclusive OR

---

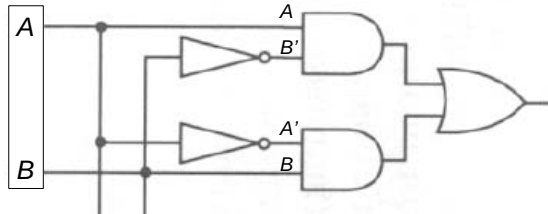


---

## The Circuit Simulator

## Exclusive OR

---

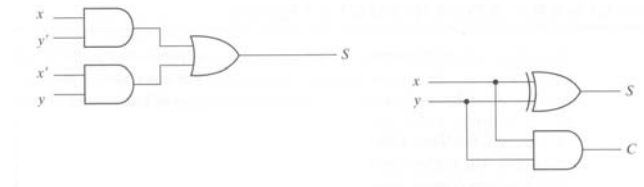


## Circuit Simulator


---

- Go to Exercise 1 on the course webpage
  - Do Exercise 1 of this page (notice that the rest of the page is the homework)
- To get started, download the Circuit Simulator (SimCir) zip file
- Select "Open Using Winzip"
- When the zip file opens, double click simcir.jar
- [Circuit Simulator](#) link

## Circuit Simulator Window

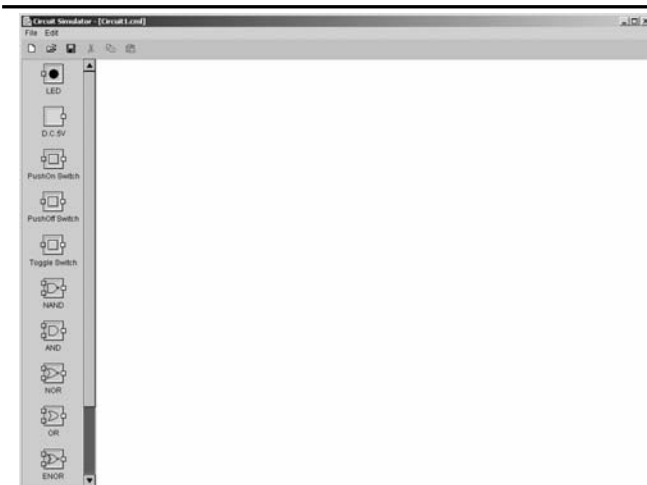

## Circuit Example

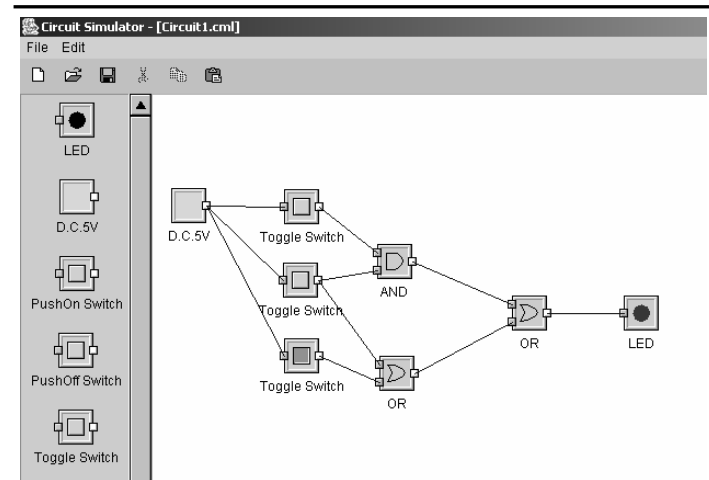

## Using the Simulator

- Include a power supply (only need one)
- Use toggle switch for inputs
- Use LED for output (red=1, black=0)
- Quirks
  - If you resize, it will jumble your circuit
  - To cut – select, and then click on the scissors
  - Some people have trouble saving – test this first!!

Onto the  
Adder Circuit...

## Addition

- Adding decimal numbers

- Concept of the carry digit

15

27

42

- Adding binary numbers

- Concept of sum and carry bits

## Addition Concepts

- Two inputs – two numbers to add, digit by digit (bit by bit)
  - *AND*, there is a carry, which we represent as a third input
- Two outputs
  - Sum
  - Carry
- ‘Carry’ is an output from one step, and an input to the next one

## Binary Addition

- Add

- $0 + 0 =$

- $0 + 1 =$

- $1 + 0 =$

- $1 + 1 =$

- Add these numbers

c:

1000111

1011010

1011010

0100110

1000111

0111001

s:


## Binary Addition: Half Adder

- We need a circuit to add two bits
  - Either bit can be ‘0’ or ‘1’
- The function in the truth table is
  - Sum =  $A'B + AB'$
  - Carry =  $AB$

| <i>A</i> | <i>B</i> | Sum | Carry |
|----------|----------|-----|-------|
| 0        | 0        | 0   | 0     |
| 0        | 1        | 1   | 0     |
| 1        | 0        | 1   | 0     |
| 1        | 1        | 0   | 1     |

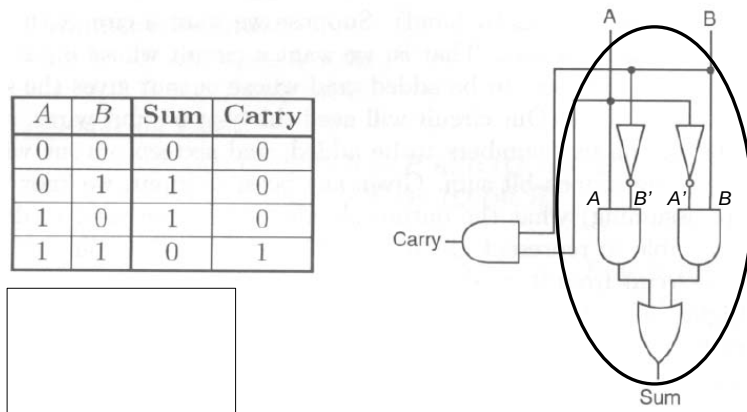
## Binary Addition: Half Adder

- A circuit with two inputs and two outputs



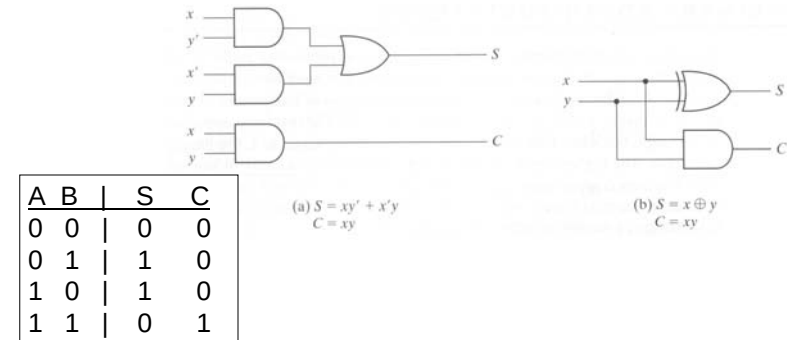
## The Half-Adder and Exclusive OR Gate

- $A'B + AB' = \text{Exclusive OR}$ 
  - Typically abbreviated to XOR
  - Simulator uses EOR



## Binary Addition: Half Adder

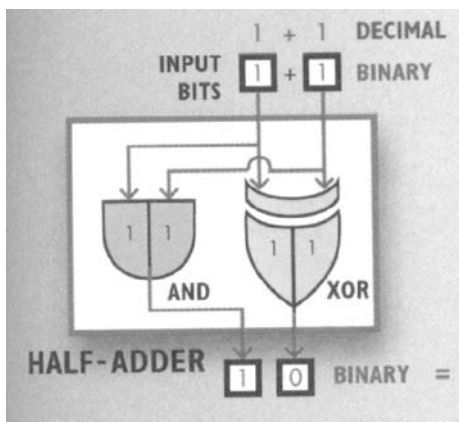

## Binary Addition: Full Adder

- A full adder is a circuit with *three* inputs (including a 'carry-in') and two outputs (the sum and carry-out)
  - What is the third input?
  - Exercise: Add 111+ 101

|              |         |
|--------------|---------|
|              | (carry) |
| 1 1 1        | ('A')   |
| <u>1 0 1</u> | ('B')   |
|              | (sum)   |


- For adding two numbers, we need three inputs


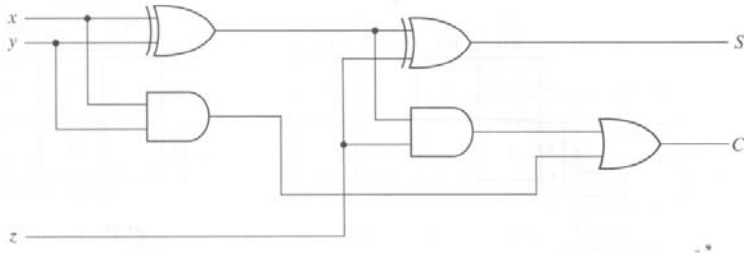
## Binary Addition: Full Adder

---

- Cascade two half-adders to get a full adder



## Summary

---

- Digital logic circuits
  - Transistors/Switches
  - Binary numbers
  - Boolean algebra
  - Propositional logic
- Primary logic functions
  - AND, OR, NOT
- Binary addition
  - Half adder circuit

## Administration

---

- Class slides will be posted
- Quiz 1 – posted, and is due at midnight Sunday.
- Office hours and TA