

Memory Circuits & the CPU

CSC 103

September 20, 2005

Overview for Today


- Memory circuits
 - The importance of feedback
 - The organization of RAM
 - Control signals – R/W & Select
 - Data signals – a single shared data bus
- The CPU – central processing unit
 - Fetch-execute cycle
 - The Pippin simulator

Memory Circuits & Feedback

Physical Wiring of RAM

- Data bus
 - The single data bus is connected simultaneously to all locations in RAM
 - The data bus is for data input *and* data output
- Control
 - ‘Select’ specifies which address/location to read or write
 - ‘R/W’ specifies whether the location will be read or written

Memory Array

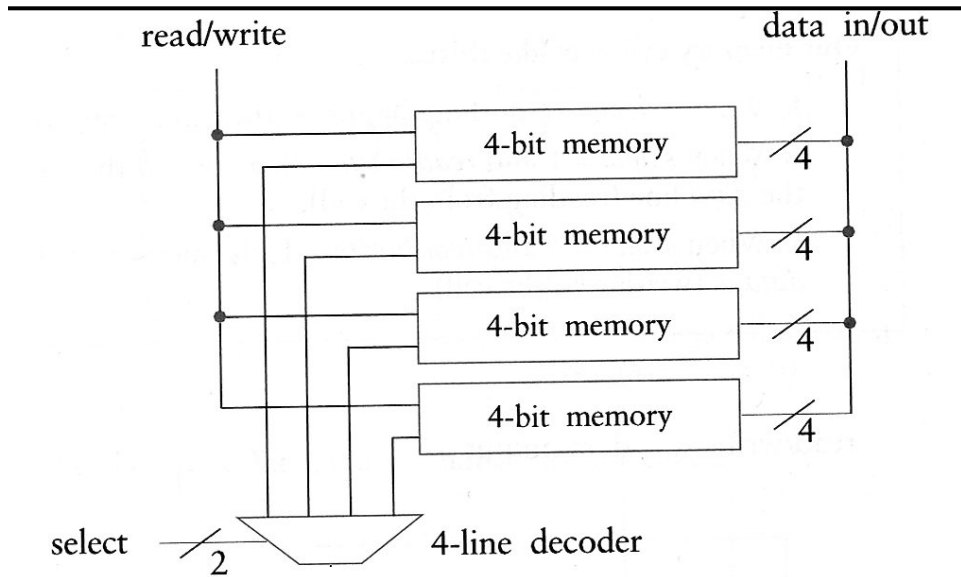



Memory Array Construction

- Build a 1-bit memory cell
- Connect 1-bit cells to the 'word' size desired
 - Word = 4 bits in class examples
 - Word = 64 bits on new Pentiums
- Include control lines to each word
 - Select – the location
 - Read/write
- Include data bus connection to each word

1-Bit Memory Circuit

- Memory circuit
 - Two possible *states*, '1' and '0'
 - Store or remember the state by maintaining the output at either '1' or '0'
 - If we control which value is stored then we have a memory (RAM) circuit
- Trace the behavior of the circuit when...
 - If both inputs are 'off' and initial state is 'off'
 - If both inputs are 'off' and initial state is 'on'

1-Bit Memory Circuit

  


The Concept of Feedback

- The output of a circuit is fed-back to the input
- Important category of circuits for which looking at the inputs *does not* tell you the value of the output
- §2.3, page 58 onward

 
Problems With Simple Memory Circuit

- Building up to our initial memory ‘array’ figures...




- We do not have control over *when* data is stored or read
 - Each cell must be read or written to *only when* its unique address is selected

1-Bit Memory: Load Control

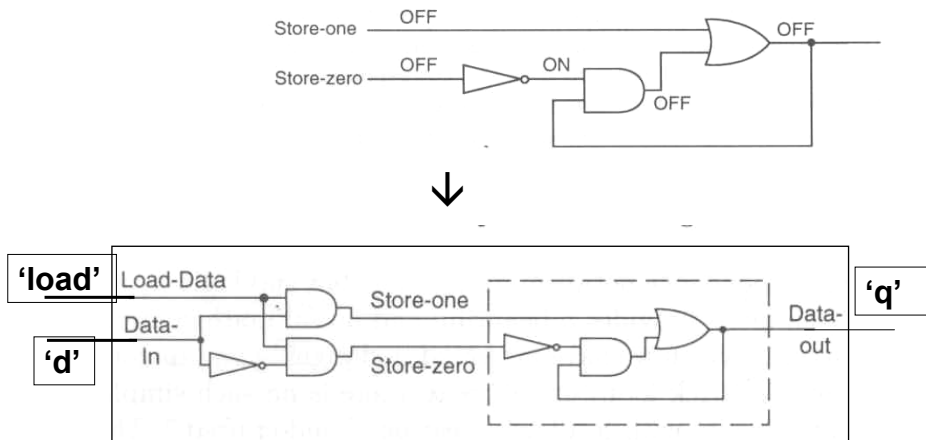


1-Bit Memory: R/W, Select, Data Bus

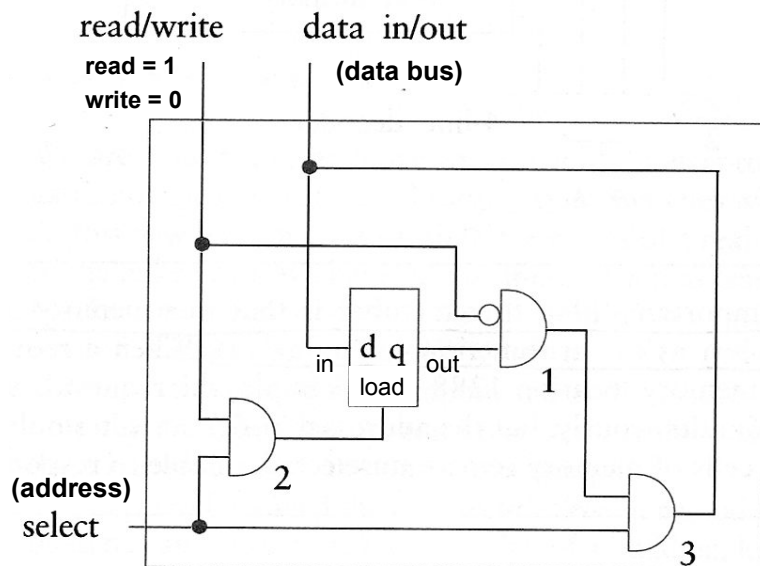


Behavior of 1-Bit Memory Cell

- When $select = 0$, nothing happens (the cell is inactive)
- When $select = 1$ **and** $read/write = 0$, a copy of the stored bit is put on the data bus (reading from the cell)
- When $select = 1$ **and** $read/write = 1$, the data on the data bus is stored into the cell (writing to the cell)

Cascaded 1-Bit Memory Cells

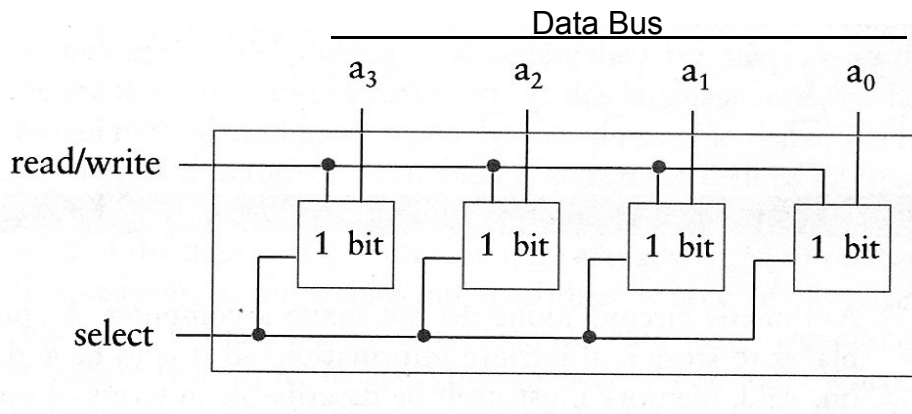

Memory Array

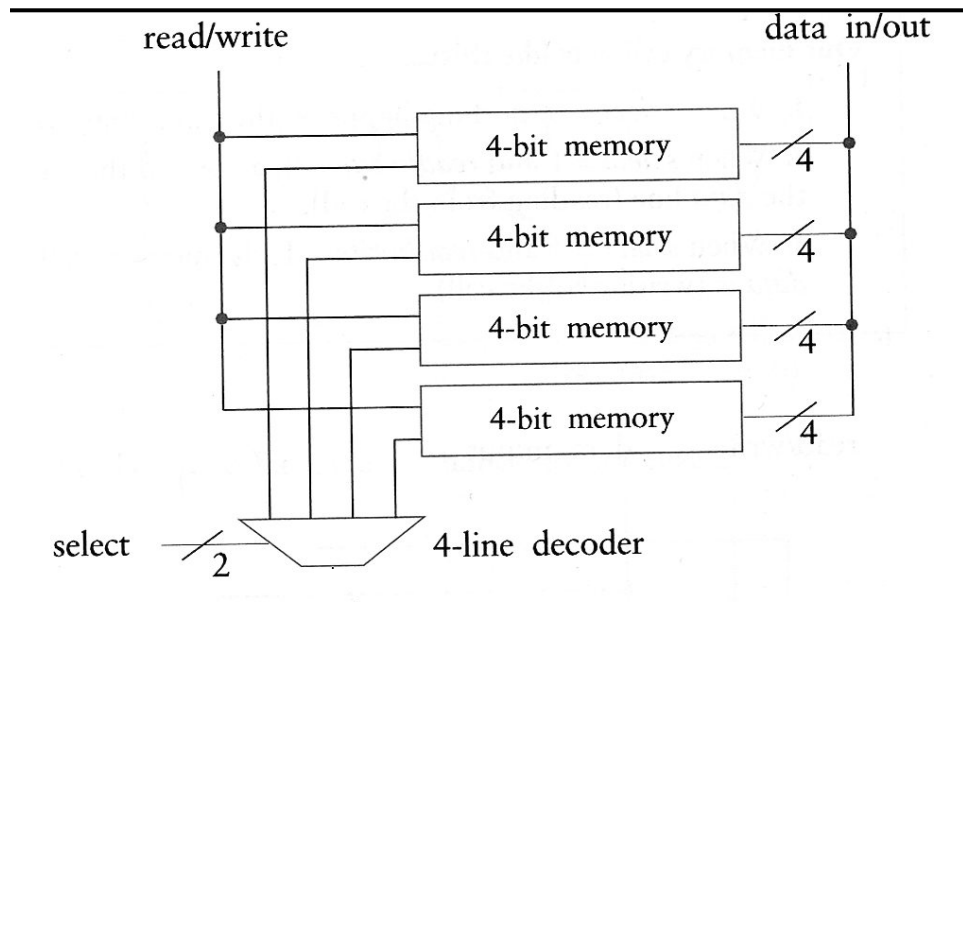

The CPU &
'Fetch-Execute'

Computer Operation

- Computer *only* execute programs
- Programs are sequences of instructions
- To execute programs the computer
 - **Fetches** the next instruction, and any data needed
 - **Executes** the instruction
- This is the ‘fetch-execute’ cycle

Addition Example

To perform $2 + 3 = 5$:

1. Load ‘2’ into the CPU
2. Add ‘3’ to ‘2’ and temporarily store the result, ‘5’
3. (=) Store the result to main memory

‘Fetch’ each instruction and data, and then do what it directs

Addition Example Con't

- Keeping everything organized
 - The CPU must know where to find everything
 - Data and instructions
 - The CPU must know where to store the result

Components of Pippin

- Pippin handout
 - ALU
 - Registers
 - PC, the program counter
 - Instruction register
 - Accumulator (the computer's scratch pad)
 - Decoder
 - MUX
 - RAM

Addition Example Con't

- Keeping everything organized
 - The CPU must know where to find everything
 - Data and instructions
 - The CPU must know where to store the result
- Performing the example in *binary*!
 - The operations (*e.g.*, 'ADD') need a binary number assigned to them
 - The operands (data) must be in binary

Assembly Language

- Our example must be written in simple steps
 - LOD #2 = load #2 into the CPU
 - ADD #3 = add #3 to whatever is there
 - STO Y = store the result to 'Y'
 - HLT = stop!

TA Times

- TA: Allison Bellew
 - Meet in McConnell 104
 - Sunday 7-9 pm
 - Monday 6-7 pm

Summary

- Memory
 - 1-bit storage & feedback
 - Control lines: R/W and select (address)
 - Data bus
- The CPU
 - The fetch-execute cycle
 - The Pippin CPU simulator