

# Circuit Theory Analysis: The Map of Maps

- a) Understand the flow of electricity in a variety electrical circuits
- b) Begin to understand the flow of electrical energy in all electrical systems or media

## Map 1: Electrical Circuit Structure

Determine the significant aspects of the circuit (source, elements & topology) and determine the category, or type, or circuit as well as what you expect for circuit behavior.

Circuit structure (page 1 below) consists of one or more sources of electrical energy and circuit elements such as resistors, capacitors, inductors and transistors. These elements can be connected in innumerable patterns, typically recognized as series and parallel connections, further identified as branches, nodes and loops.


## Map 2: Electrical Circuit Behavior

Given your expectations for the circuit behavior, identify the values you need to calculate, select the specific analysis methodology(s) and proceed to calculate the required values.

Circuit behavior (page 2 below) is determined by the sources, elements and topology. Visual inspection of the circuit will guide you, the analyst, in knowing what to expect for the circuit behavior (with practice and experience!)
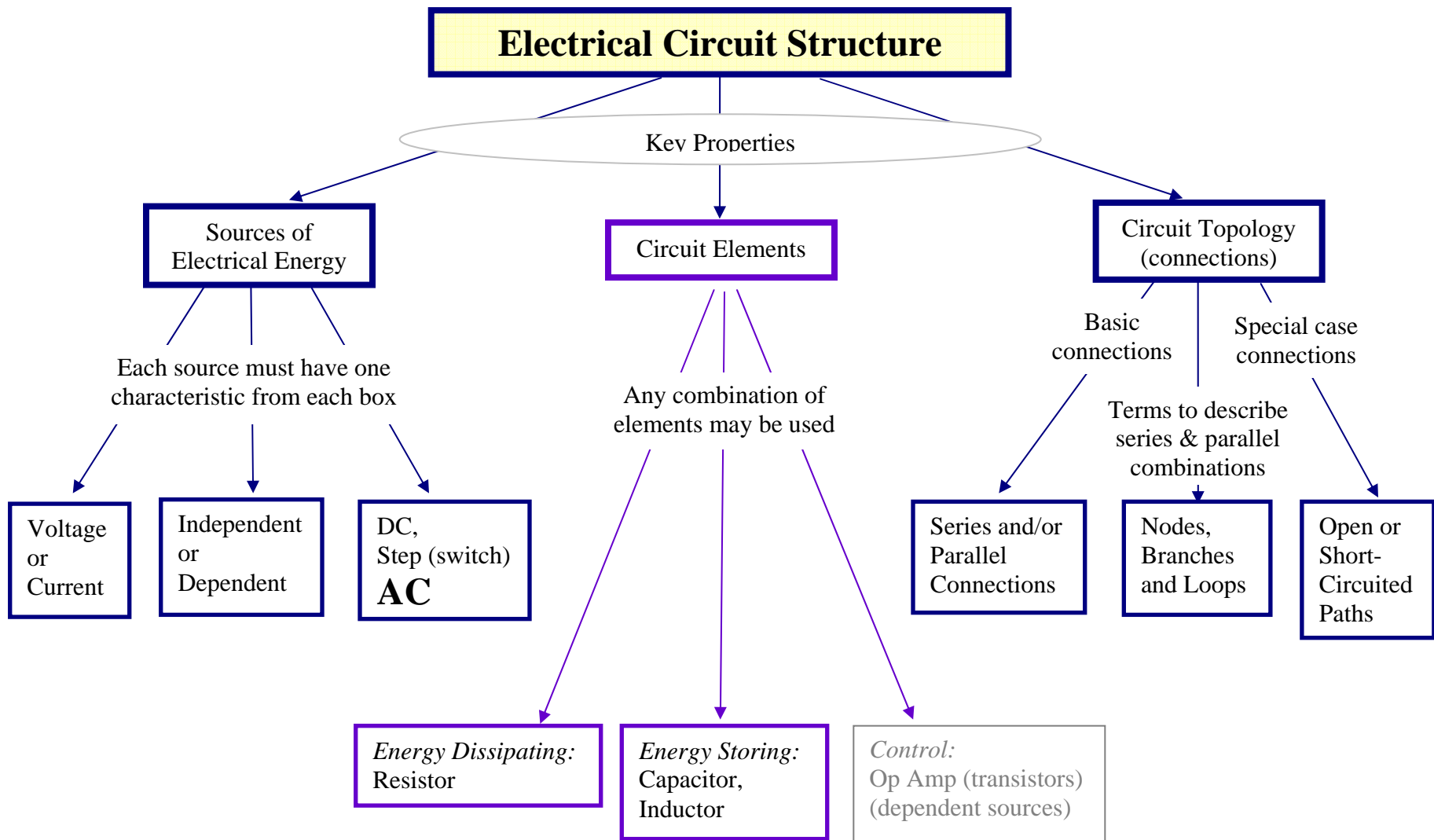
## Map 3: Electrical Circuit Analysis

Throughout EGR 220, you will learn circuit analysis (page 3 below) methodologies that build upon each other, providing you with all the basic tools to analyze any linear electrical circuit. In some situations, more than one methodology is appropriate, while in others there is clearly a best analysis tool.



# Electrical Circuit Analysis

General Technique: Identify & Reduce Complexity

## DC Circuits

Ohm's Law  
Resistors in series & parallel  
Kirchhoff's Voltage & Current Laws (**Conservation Laws**)  
Nodal & Mesh Analysis  
**Linearity**, Superposition & Source Transformation  
**Equivalence**: Thevenin & Norton's Theorems

## Circuits with Storage and Switches

Step response  
Total Response = Natural + Forced Response ( = *transient* + *steady state response* )  
→ Introduces **differential equations**, the **exponential** & oscillatory response

## AC Circuits

Time domain analysis  
Phasors, **Complex numbers** & the Complex plane  
Power and Power Systems (**RMS**)  
Frequency response and the frequency domain  
(**Transformations** & Bode plots)

## General Circuits

Two-Port Networks

Analysis Techniques for Circuits of Increasing Complexity

\* **Red Text** indicates key mathematical concepts

- Objective
- Quantify the voltage and current waveforms for every element
  - Quantify the energy and power for each element and the entire circuit






# Electrical Circuit Behavior

Input, Sources

System, Circuit Composition

Output, Circuit Behavior

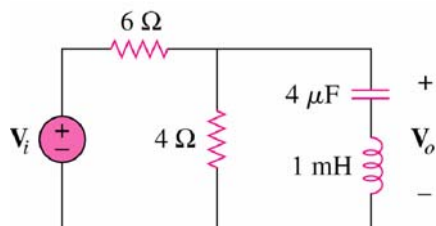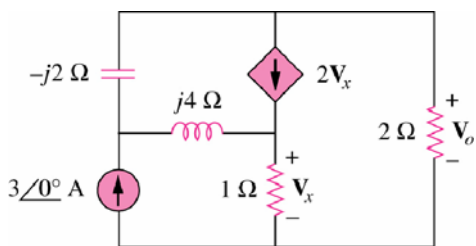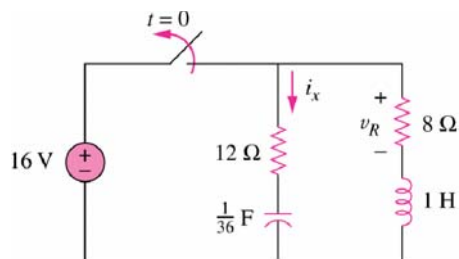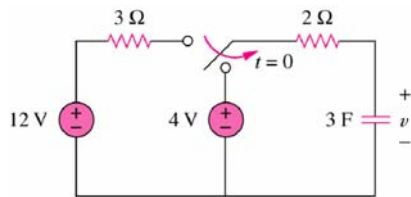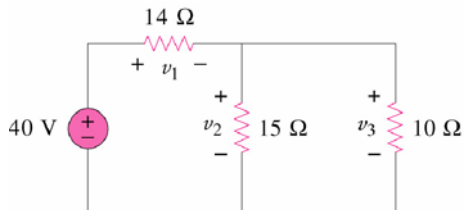Each circuit below exhibits one of the behaviors on the right.



$$H(s) = \frac{200s}{(s+2)(s+10)}$$

DC (static)

First Order Circuit

Second Order Circuit

Phasors: SSS

Multiple  $f$  input (Bode plot)

