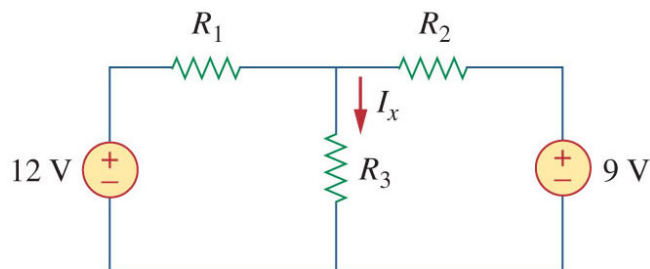


You Do NOT need to hand this homework in – but be able to do the problems. These concepts will be on Exam 1 (Feb 19<sup>th</sup> during Lab Time)


### Chapter 3 Problems

- 1) Find  $i_x$  in the circuit below. You must select R values (select simple values, but not all =  $1\Omega$ )




- 2) Solve for  $V_1$  in the circuit below (circuit for problems 2 & 3), using nodal analysis

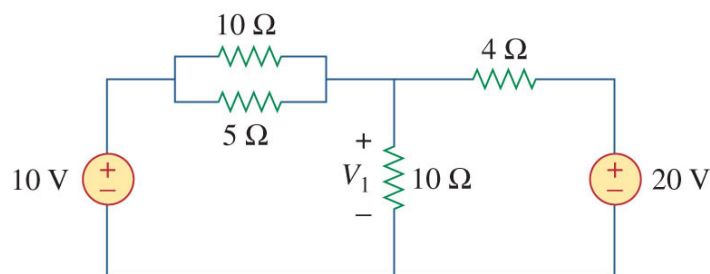
- 3) Solve for  $V_1$  in the same circuit below, using **mesh** analysis



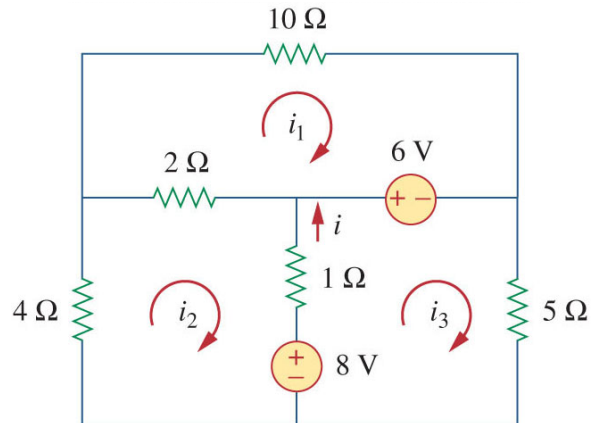4) Solve for  $i$  in the circuit below using **mesh** analysis.




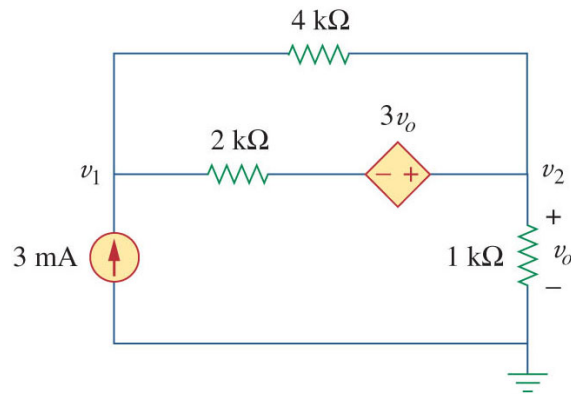5) Find  $v_1$  and  $v_2$  in the circuit below, using nodal analysis.




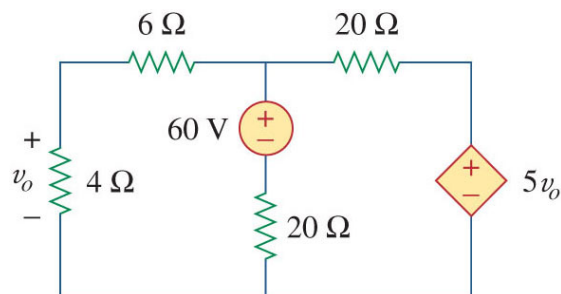6) Using Nodal Analysis, find  $v_o$ . Things to notice about this circuit:


- There is a dependent source – a voltage source that depends upon a different voltage value for its own value. This occurs in real circuits where there are transistors in the circuit
- The 60V source is not connected to ground, which means it contributes a 60V increase in voltage potential, with respect to the voltage that is at the node shared with the 20Ω resistor.



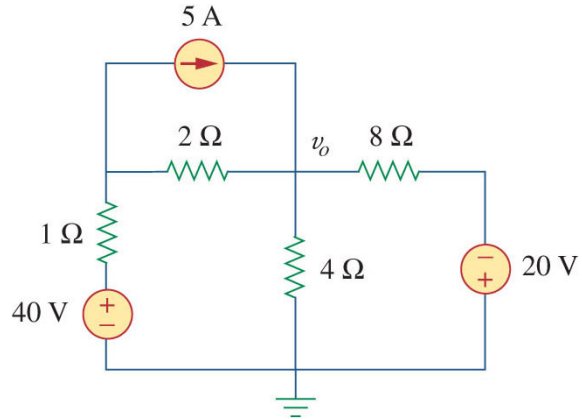7) Using Mesh Analysis, find  $v_o$  in the circuit below.



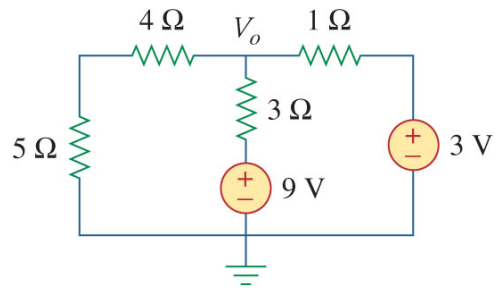8) Use *superposition* to find  $V_o$  in the circuit below.



**Extra**

Use **source transformation** to find  $V_o$  in the circuit above (from problem 8)