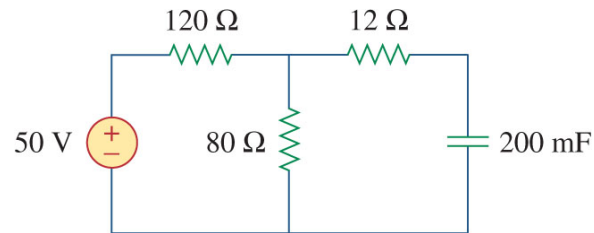
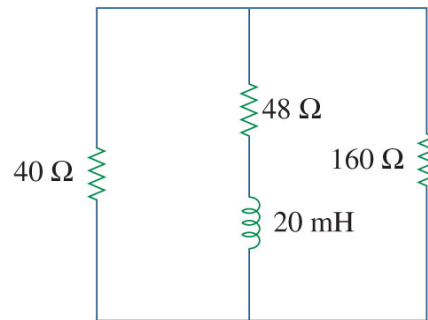


**Problem 1:**


Find the time constant for the circuit below.

**Problem 2:**

Find the time constant for the circuit below.


**Problem 3:**

Find the voltage across the capacitors in the circuit below under dc conditions.

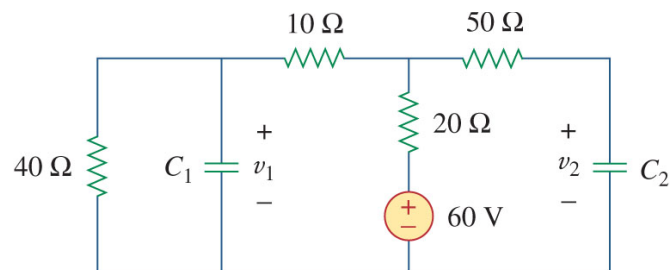

**Problem 4:**

Find  $v_C$  and  $i_L$  in the circuit below, under dc steady-state conditions.

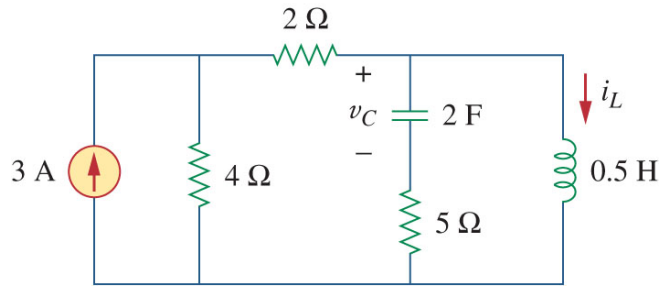**Problem 5:**

A 100-mH inductor is connected in parallel with a 2kΩ resistor (source-free circuit).


The current through the inductor is  $i(t) = 50e^{-400t} \text{ mA}$

- Find the voltage  $v_L$  across the inductor.
- Find the voltage  $v_R$  across the resistor.
- Does  $v_L + v_R = 0$ ? Provide a brief explanation along with yes/no.
- Calculate the current through the inductor at time  $t = 5$  seconds.

**Problem 6:**

The switch has been closed for a long time, and it opens at time  $t = 0$ .

- Find  $v(t)$  for time  $t \geq 0$ .
- Sketch and label a graph of  $v(t)$  vs.  $t$ .

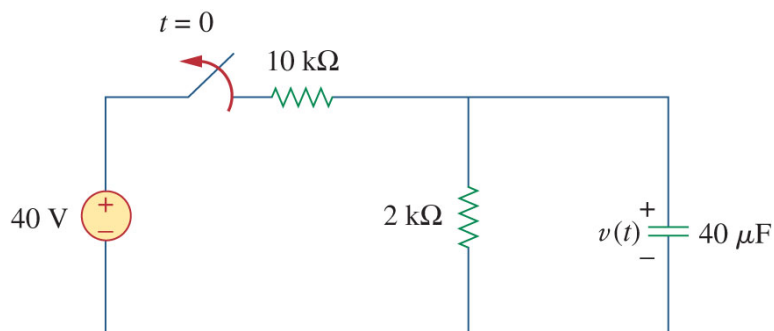

**Problem 7:**

A circuit is described by the differential equation:

$$4 \frac{dv(t)}{dt} + v(t) = 10$$

- What is the time constant of this circuit?
- What is  $v(\infty)$ , the final value of  $v(t)$ ?
- If  $v(0) = 2$ , find  $v(t)$  for  $t \geq 0$ .
- Sketch and label a graph of  $v(t)$  vs.  $t$ .

Note that there is a short discussion in the text on referring a 'describing equation' (*i.e.*, the differential equation) to an actual circuit.

**Problem 8:**

A simple relaxation oscillator circuit is shown below. The neon lamp fires when its voltage reaches 75 V and turns off when its voltage drops to 30 V. The lamp's resistance is  $400\Omega$  when on and infinitely high when off.

- For how long is the lamp on for each period that it is on?
- What is the time interval between light flashes?

