

Chapter 7, Solution 79.

When the switch is in position 1, $i_o(0) = 12/3 = 4\text{A}$. When the switch is in position 2,

$$i_o(\infty) = -\frac{4}{5+3} = -0.5\text{A}, \quad R_{Th} = (3+5)//4 = 8/3, \quad \tau = \frac{L}{R_{Th}} = 3/80$$


$$i_o(t) = i_o(\infty) + [i_o(0) - i_o(\infty)]e^{-t/\tau} = \underline{-0.5 + 4.5e^{-80t/3}}\text{ u(t)A}$$

GRAPH: (included at end) The important elements to label on the graph are:

- the axes
- the initial and final values
- the time constant, which is where $i(t)$ is at $\sim 37\%$ of its maximum value

Chapter 7, Solution 90.

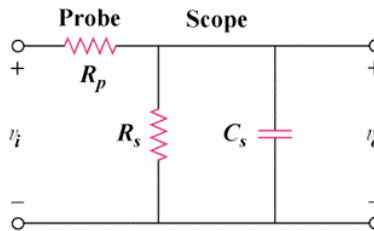You can approach this problem as a design problem for the oscilloscope probe \rightarrow you want to design the 'scope probe, which is to say determine values for R_s and C_s , such that the voltage v_o is $0.1v_i$.



Use the voltage divider to find the voltage across R_s , which is equal to v_o . For the *time constant* you know that the equivalent resistance is that from the nodes of the capacitor, and is equal to R_{eq} .

$$v_o = v_i \frac{R_s}{R_s + R_p}, \quad R_{eq} = R_s \parallel R_p$$

From the design criteria, we know

$$v_o = \frac{1}{10} v_i \quad \longrightarrow \quad \frac{1}{10} = \frac{R_s}{R_s + R_p}$$

Combining these, along with the information in the problem statement:

$$R_s = \frac{1}{9} R_p = \frac{6}{9} = \underline{\underline{\frac{2}{3} \text{ M}\Omega}}$$

We are also given that,

$$\tau = R_{eq} C_s = 15 \mu\text{s}$$

Finally, you can solve for C_s : $R_{eq} = R_p \parallel R_s = \frac{6(2/3)}{6 + 2/3} = 0.6 \text{ M}\Omega$

$$C_s = \frac{\tau}{R_{th}} = \frac{15 \times 10^{-6}}{0.6 \times 10^6} = \underline{\underline{25 \text{ pF}}}$$

Chapter 8, Solution 17.

Find the initial conditions and α and ω_o , and identify the type of damping (the form of the mathematical expression for the natural response).

$$i(0) = I_o = 0, \quad v(0) = V_o = 4 \times 15 = 60$$

$$\omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\frac{1}{4} \frac{1}{25}}} = 10$$

$$\alpha = \frac{R}{2L} = \frac{10}{2 \frac{1}{4}} = 20, \text{ which is } > \omega_o.$$

Here we have an overdamped response.

Next find the roots, $s_{1,2}$ and construct the complete response. In this problem, we have a source-free response, so $i(\infty) = 0A$. Thus the complete response is the same as the natural response.

$$s = -\alpha \pm \sqrt{\alpha^2 - \omega_o^2} = -20 \pm \sqrt{300} = -20 \pm 10\sqrt{3} = -2.68, -37.3$$

$$v(t) = A_1 e^{-2.68t} + A_2 e^{-37.3t}$$

To find a numerical value for dv/dt at $t=0$, use the fact that $i_c = C(dv/dt)$. In this circuit we see that $i_c = i_L$, so:

$$\left. \frac{dv(t)}{dt} \right|_{t=0} = \left. \frac{i_c(t)}{C} \right|_{t=0} = \left. \frac{i_L(t)}{C} \right|_{t=0} = 0 \text{ V/s}$$

Now use the initial conditions to solve for the constants, A_1 and A_2 .

$$v(0) = 60 = A_1 + A_2$$

$$\left. \frac{dv(t)}{dt} \right|_{t=0} = 0 = -2.68A_1 - 37.3A_2$$


The final solution is:

$$\boxed{v(t) = (64.6e^{-2.68t} - 4.64e^{-37.3t}) \text{ V}}$$

Chapter 8, Solution 21.

By combining some resistors, the circuit is equivalent to that shown below.
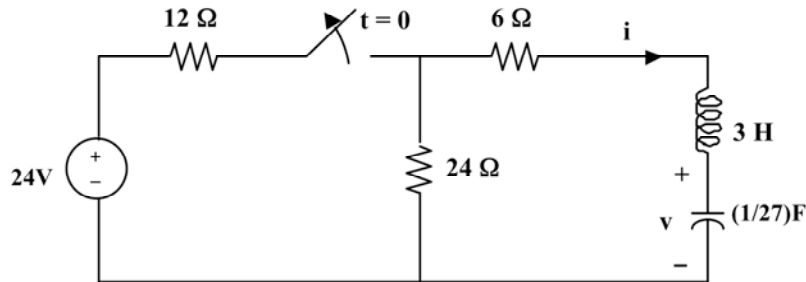
$$60 \parallel (15 + 25) = 24 \text{ ohms.}$$



At $t = 0^-$, $i(0) = 0$, $v(0) = 24 \times 24 / 36 = 16\text{V}$

We also can find $dv(t)/dt$ for time $t = 0$. As above, we find

$$\left. \frac{dv(t)}{dt} \right|_{t=0} = \left. \frac{i_c(t)}{C} \right|_{t=0} = \left. \frac{i_L(t)}{C} \right|_{t=0} = 0\text{V/s} = \left. \frac{dv_c(0)}{dt} \right|_{t=0}$$

** It is **VERY** important to know that it is only in simple series RLC circuits, in this case for $i_c = i_L$ and the open circuit behavior of the capacitor makes $i_L = 0$, that we can use $i_c = 0$. This is often *not the situation*.

For $t > 0$, we have a series RLC circuit. $R = 30$ ohms, $L = 3$ H, $C = (1/27)$ F

$$\alpha = R/(2L) = 30/6 = 5$$

$$\omega_o = 1/\sqrt{LC} = 1/\sqrt{3 \times 1/27} = 3, \text{ clearly } \alpha > \omega_o \rightarrow \text{overdamped response again}$$

Find the roots:

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_o^2} = -5 \pm \sqrt{5^2 - 3^2} = -9, -1$$

Again, with a source-free problem, we have the natural response = complete response, =

$$v(t) = [A_1 e^{-t} + A_2 e^{-9t}]$$

Using the initial conditions, solve for A_1 and A_2

$$v(0) = 16 = A_1 + A_2$$

$$\left. \frac{dv(t)}{dt} \right|_{t=0} = \left. \frac{dv(0)}{dt} \right|_{t=0} = 0 = -9A_1 - A_2$$

To find the final solution: $\boxed{v(t) = (18e^{-t} - 2e^{-9t}) \text{ V}}$

Chapter 8, Solution 24.

When the switch is in position A, the inductor acts like a short circuit so

$$i(0^-) = 12 \text{ A}$$

When the switch is in position B, we have a source-free parallel RCL circuit

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 10 \times 10 \times 10^{-3}} = 5$$

$$\omega_o = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\frac{1}{4} \times 10 \times 10^{-3}}} = 20$$

Since $\alpha < \omega_o$, we have an underdamped case.

$$s_{1,2} = -5 + \sqrt{25 - 400} = -5 + j19.365$$

$$i(t) = e^{-5t} (A_1 \cos 19.365t + A_2 \sin 19.365t)$$

$$i(0) = 12 \text{ A} = A_1$$

$$v = L \frac{di}{dt} \longrightarrow \frac{di(0)}{dt} = \frac{v(0)}{L} = 0$$

$$\frac{di}{dt} = e^{-5t} (-5A_1 \cos 19.365t - 5A_2 \sin 19.365t - 19.365A_1 \sin 19.365t + 19.365A_2 \cos 19.365t)$$

$$0 = di(0)/dt = -5A_1 + 19.365A_2 \text{ which leads to } A_2 = (5A_1)/19.365 = 3.098$$

Thus,

$$i(t) = e^{-5t} (12 \cos(19.365t) + 3.098 \sin(19.365t)) \text{ A}$$

GRAPH: (included at end) The important elements to label on the graph are:

- the axes
- the initial and final values
- the oscillations, with the frequency of ω_d labeled
- the exponential decay of $e^{-\alpha t}$ 'envelope' superimposed upon the oscillatory response

Chapter 8 Problem 49

This problem has a step input for the input function, meaning that you must solve for the *complete solution*, and not simple for the natural response as for the source-free circuits.

$$\text{For } t = 0^-, i(0) = 3 + 12/4 = 6 \text{ and } v(0) = 0.$$

For $t > 0$, we have a parallel *RLC* circuit with a step input.

$$\alpha = 1/(2RC) = (1)/(2 \times 5 \times 0.05) = 2$$

$$\omega_0 = 1/\sqrt{LC} = 1/\sqrt{5 \times 0.05} = 2$$

Since $\alpha = \omega_0$, we have a critically damped response.

$$s_{1,2} = -2$$

Thus the complete response is of the form:

$$i(t) = I_\infty + [(A + Bt)e^{-2t}], \quad I_\infty = 3$$

Now use the initial conditions to solve for the constants:

$$i(0) = 6 = 3 + A \text{ or } A = 3$$

$$v = L di/dt \text{ or } v/L = di/dt = [Be^{-2t}] + [-2(A + Bt)e^{-2t}]$$

$$v(0)/L = 0 = di(0)/dt = B - 2 \times 3 \text{ or } B = 6$$

$$\text{Thus, } \boxed{i(t) = 3 + [(3 + 6t)e^{-2t}] \text{ A}}$$

Problem 7: Discuss behavior of 1st & 2nd order, and compare/contrast → options**First Order**

- Exponential behavior representing the energy storage element charging and/or discharging energy
- The time constant quantifies the amount of time for charging and discharging

Second Order

- Circuit behavior representing the two energy storage elements exchanging the stored energy, combining charging and/or discharging behavior
- Represented as a sum of exponentials
- There may be oscillation with two energy storage elements, but the resistance in the circuit may damp it out
- The circuit behavior can be characterized by the natural frequency and the damping coefficient, or equivalently, but the two natural frequencies

Compare 1st and 2nd order

- Both have underlying exponential behavior – single exponential or sum of 2
- Only 2nd order (or higher order) circuits may have oscillatory behavior.
- Both types of circuits have initial conditions, final conditions and transient, or natural behavior to move between these two steady-state conditions

HW 8 graphs


7.79)

$i(t)$
(amps)

$I_0 = 4$

1.2

$I_{\infty} = -\frac{1}{2}$

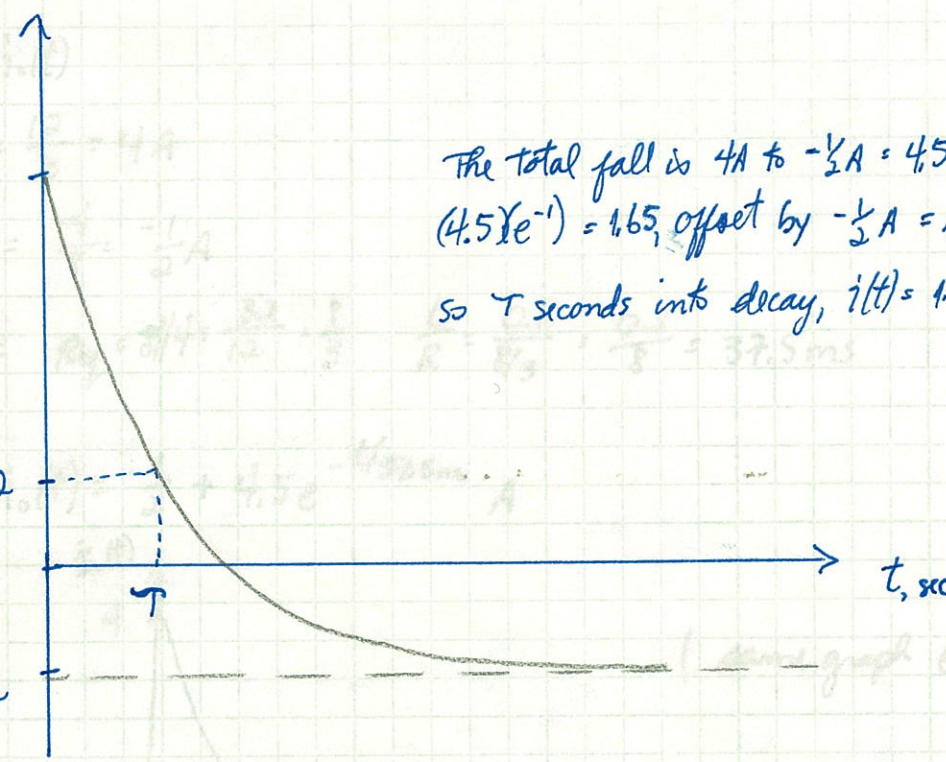


The total fall is $4A$ to $-\frac{1}{2}A = 4.5A$
 $(4.5)e^{-t} = 1.65$, offset by $-\frac{1}{2}A = 1.2A$
 so T seconds into decay, $i(t) = 1.2A$

8.24)

$i(t)$
Amps

$I_0 = 12A$

$I_{\infty} = 0A$

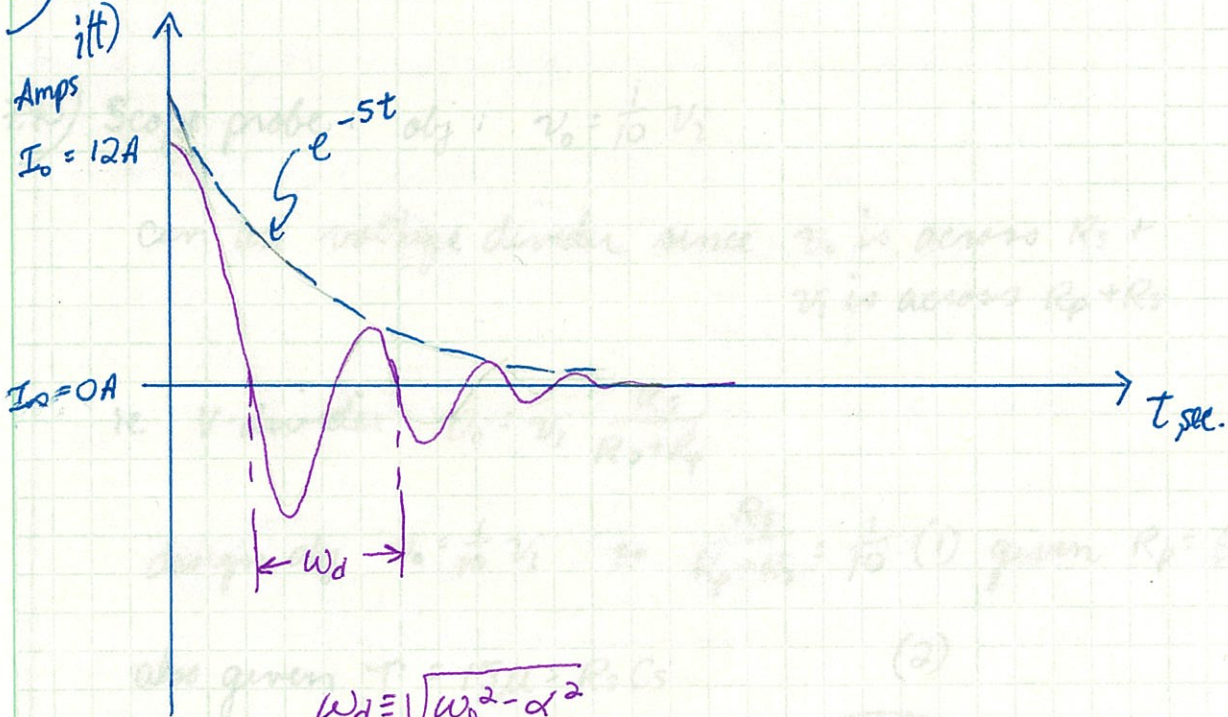

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

from (1) find $R_3 = R_4 = 6M$ so $R_3 = 3M$

from (2) find $C_3 = \frac{15\mu}{3/6M} = \frac{15\mu}{0.5M} = 30\mu$ $25pF$