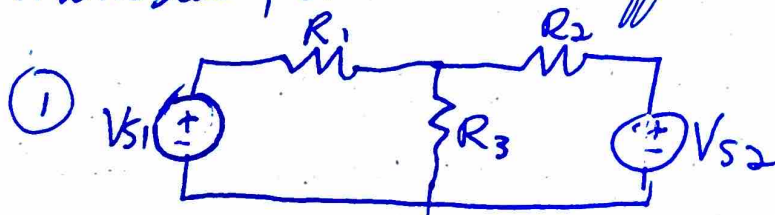


Note for superposition, you analyze the circuit with one source active at a time, and all other sources set equal to zero


★ For a Voltage source $0V$ is a short circuit
For a current source $0A$ is an open circuit

From lab, teams did different experiments




a) finding V_{R3} → class example

b) finding I_{R3}

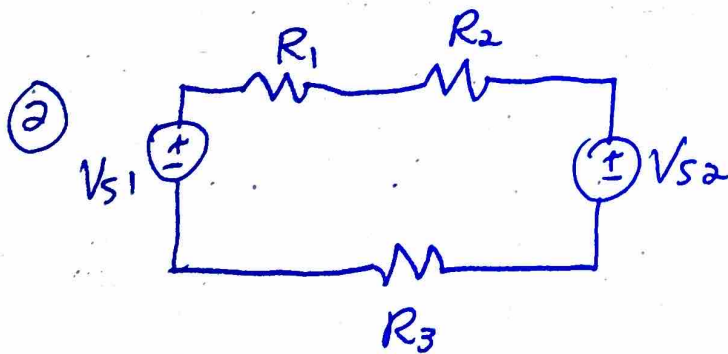


a) finding V_{R2}

I_{R3}

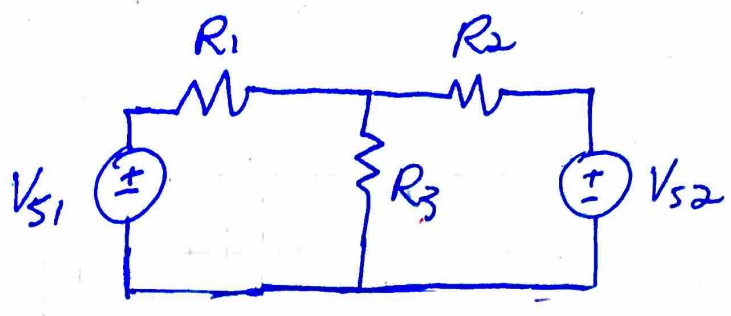

to find I_{R3}

step 1

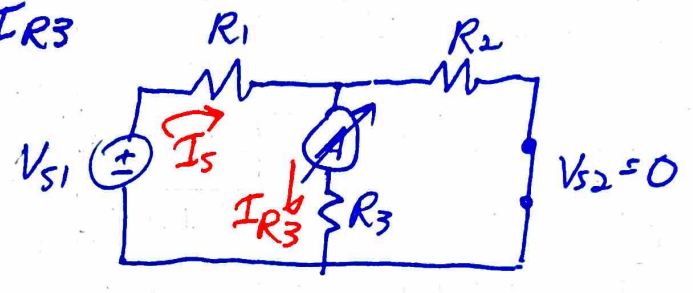

$$R_{eq} = R_1 + R_2 \parallel R_3$$

$$I_s = \frac{V_{s1}}{R_1 + R_2 \parallel R_3}$$

THEN USE CURRENT DIVIDER


REMEMBER $I_{R3} \propto R_2$

$$I_{R3} = I_s \left(\frac{R_2}{R_2 + R_3} \right)$$



so ~~$I_{R3} = I_s \left(\frac{R_3}{R_2 + R_3} \right)$~~

Repeat with V_{s2} on & $V_{s1} = 0$

Add results for total I_{R3}

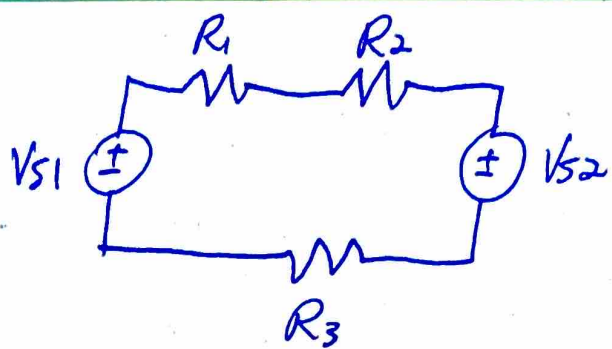


for V_1 on and $V_2 = 0V$

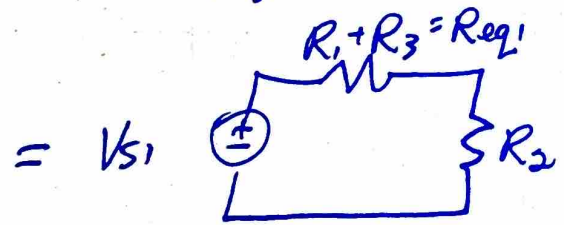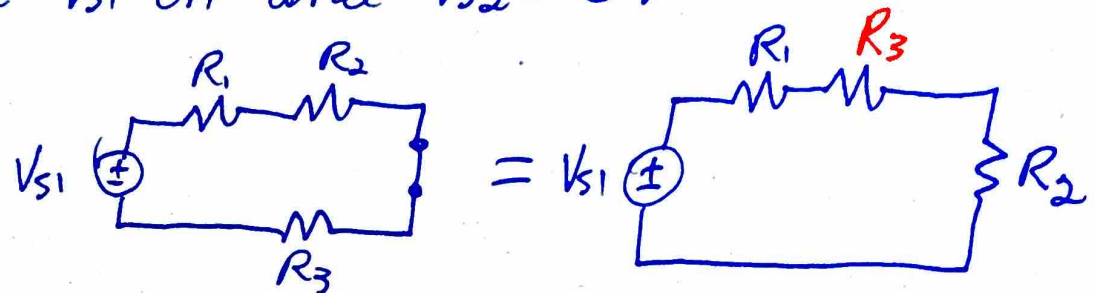

$$\text{Then } V_{R2} = V_1 \left(\frac{R_2}{R_1 + R_3 + R_2} \right)$$

Repeat with V_2 on and $V_1 = 0$

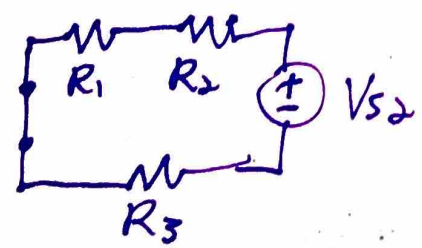

$$V_{R2} = V_2 \left(\frac{R_2}{R_1 + R_2 + R_3} \right)$$

And the total V_{R2} is the sum of the values found above