

EGR 220: Engineering Circuit Theory

Lab 4: Explore Equivalent Circuits

Theme: Equivalent Circuits & Equivalence

In class we have defined ‘equivalent’ to indicate that two circuits have the same open-circuit voltage, V_{oc} , and short-circuit current, I_{sc} , across specified terminals $a-b$. We say this means that the two circuits have the same, or equivalent, behavior at terminals $a-b$.

Possible Experiments

- 1) Remember that you are encouraged to explore and analyze circuits during lab that will help improve your understanding of one or more of our Questions of Understanding
 - a. You can pursue your own topic if you have a burning question of your own.
- 2) If you don't have your own topic to explore, since we have been working on Thevenin equivalent circuits in class, this could be a starting point for this week's lab.
- 3) You could, for example:
 - a. Design a circuit with a few resistors and a voltage source from lab power supply. As always, you can get ideas for circuits to build from the text, remembering that you need to use $k\Omega$ valued resistors (or higher).
 - b. Determine what the theoretical Thevenin equivalent is of this circuit.
 - c. Then build this Thevenin equivalent circuit also.
 - d. Measure and compare the open-circuit voltage and short-circuit current for both circuits (recall, as with the previous lab, you can have two different voltages supplied from the lab power supply by using the 6V terminals and the +25V terminals).
 - e. **OR**, as mentioned in class, you could set up these two circuits, conceal your circuits and the output level from the power supply, and then have a neighboring lab team measure the open-circuit voltage and short-circuit current for both circuits.

Prelab

- For the prelab, design your experiments, including
 - The circuits you will build, with all element values indicated
 - What you will measure, and why
 - What you expect or hope to find (measurements and/or theory) so you will be alerted if you start getting unexpected results
 - The Question(s) of Understanding you are pursuing this week.

Things you could also think about:

- 1) What did you find that confirms your ideas and theories?
- 2) What was unexpected?
- 3) Do you have new questions you can pose about the concepts and theories you are investigating, that will help you deepen your understanding of circuit theory?
- 4) Do you need to reject some ideas you previously thought were true about circuit theory?

Questions of Understanding

- 1) How are voltage and current inter-related?
 - What do I understand about the theoretical and practical connections between voltage and current?

- 2) What is voltage?
 - What do I understand about the concept of voltage?
- 3) How do conservation laws apply to circuit theory?
 - What is my understanding of how conservation laws are used in circuit analysis?
- 4) What does “equivalent” mean for electrical circuits?
 - What is my understanding of how “equivalence” is used to design and analyze circuits?

Deepening your understanding, by asking, for example:

- What am I unsure about for the concept of _____?
- What is my theory to explain _____?
- Can I design circuits and analyze their behavior to test my theory?
- How can I experiment with this theory? law? concept?