



Capacitors & Inductors: Energy Storage & Release

EGR 220, Chapter 6
February 28, 2020

1

Maximum Power Transfer

$$R_{Th} = 2 + 3 + \frac{6 \parallel 12}{4} = 9 \Omega$$


$$V_{Th} = ?$$

first identify which voltage drop(s) in the circuit are V_{Th} ?

And what role does the 2Ω R play in V_{Th} ?

$V_{Th} = V_{2A \text{ source}} + V_{2\Omega R}$ because that $= V_{ab} + V_{ab} = V_{Th}$
 cannot find this directly $\rightarrow \Rightarrow 0$ because $I_{2\Omega} = 0A$ with a-b open

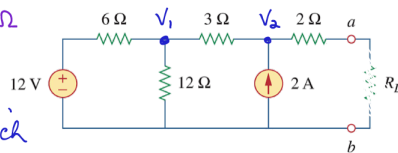so $V_{Th} = V_2$ try KCL @ V_1 & then calc V_2



3

Finish Maximum Power Transfer (ch 4)

- Useful application of the Thevenin Equivalent Circuit theory.
- Use the simplified, equivalent circuit with one voltage source and a series resistor to determine the maximum power any circuit with the equivalent characteristics can supply.
- ... the maximum power a given circuit can supply to a load.



2

2

Maximum Power Transfer

$$V_{Th} = V_2 \quad \Sigma I_{in} = \Sigma I_{out}$$


$$I_1 + I_3 = I_2$$

$$\frac{12 - V_1}{6} + 2A = \frac{V_1 - 0}{12}$$


$$\text{Find } V_1 = 16V$$

$$\text{then } V_{3\Omega} = (3\Omega)(2A) = 6V$$
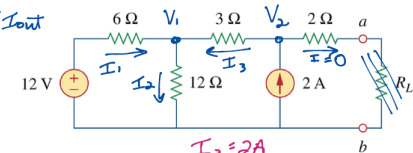
$$\text{so } V_{Th} = V_2 = 16 + 6 = 22V$$




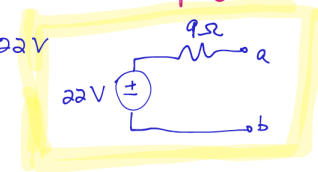$I_3 = 2A$
all 2A flows through 3Ω since a-b is open



4

Maximum Power Transfer

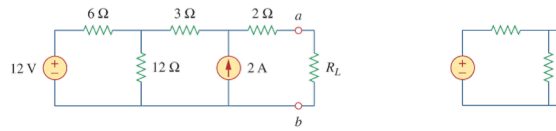

5

Overview: Energy Storage Elements

- Our questions of understanding:
 - V ; I ; conservation laws
- Energy storage and dynamics
 - Transient behavior & time constant
 - Steady-state behavior
- Introduction to capacitors
 - Matter can store electric charge
 - Create and support an electric field, E
- Introduction to inductors
 - Matter responds to moving charge (current) by inducing a voltage drop
 - Create and support a magnetic field, B




6

Filling a Bucket with Water → Time



7

Heating/Cooling a Room → Time

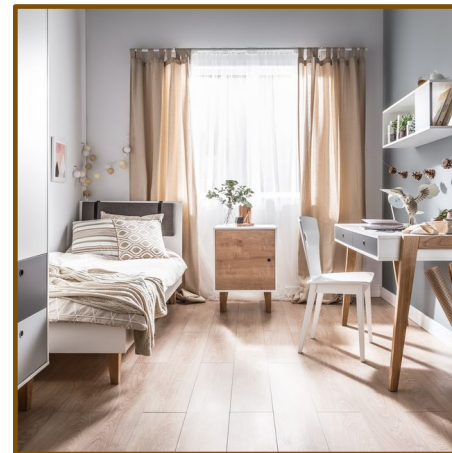

8


Natural Response → Charge & Discharge

9



Natural Response + Steady-State of Dynamic Circuits

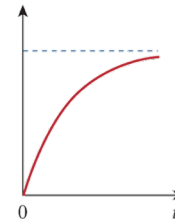- No initial stored energy, charging
- Initial stored energy, discharging
- Initial stored energy, charging




10



Natural Response + Steady-State of Dynamic Circuits

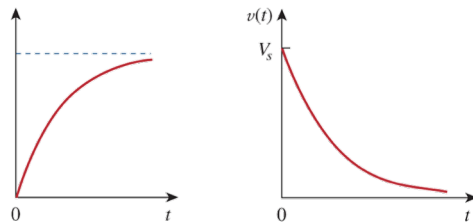- No initial stored energy, charging
- Initial stored energy, discharging
- Initial stored energy, charging




11



Natural Response + Steady-State of Dynamic Circuits

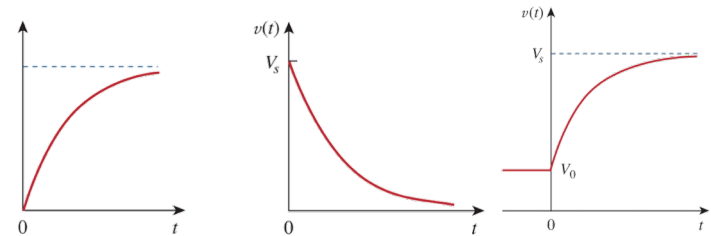
- No initial stored energy, charging
- Initial stored energy, discharging
- Initial stored energy, charging



12



Capacitors and Stored E → Voltage

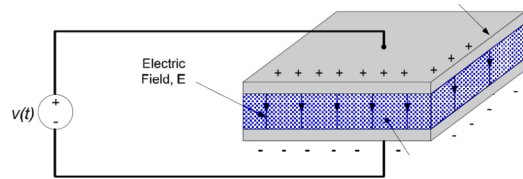


$$C \sim \frac{A}{d} \quad \& \quad C = \frac{Q}{V}$$



13

Capacitors and Stored E → Voltage

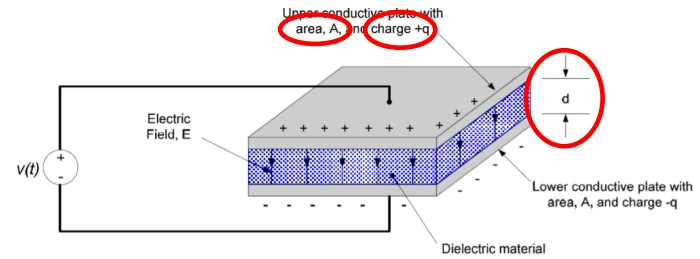


$$C \sim \frac{A}{d} \quad \& \quad C = \frac{Q}{V} \quad \rightarrow \quad Q = CV \quad \rightarrow \quad \dot{Q} = \frac{dQ}{dt} = i = C \frac{dV}{dt}$$



14

Capacitors and E-field

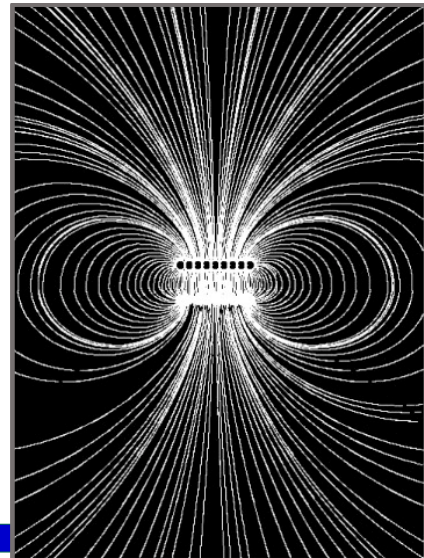

15

* Capacitors *

- Charge is stored *How? Where?*
- Expression: $q = \underline{\hspace{2cm}}$
- V-I relationship: $\frac{d}{dt} = i_c =$
- Restrictions on the voltage across a capacitor?
 - Think about calculus and taking a derivative
 - What is the steady-state behavior?



16

The 'Constituent Relations' for R, C and L


- (i.e., What is the V-I relationship?)
- R: $V_R = \underline{\hspace{2cm}}$; $I_R = \underline{\hspace{2cm}}$
- C: $V_c = \underline{\hspace{2cm}}$; $I_c = \underline{\hspace{2cm}}$
- L: $V_L = \underline{\hspace{2cm}}$; $I_L = \underline{\hspace{2cm}}$
(the dual of the expression for C)



17

17

Capacitors in Parallel: $C_{eq}=?$

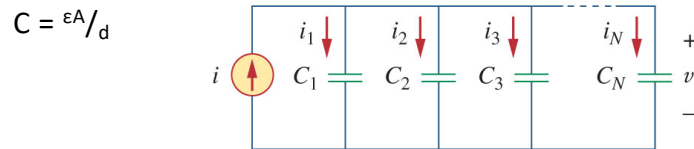

19

19

Equivalent Capacitance


- Property of 'capacitance' $C = \epsilon A/d$
- If plate area, A, increases, what happens to the capacitance?
- If the distance between the plates, d, increases, what happens to capacitance?



18

18


Capacitors in Series: $C_{eq}=?$

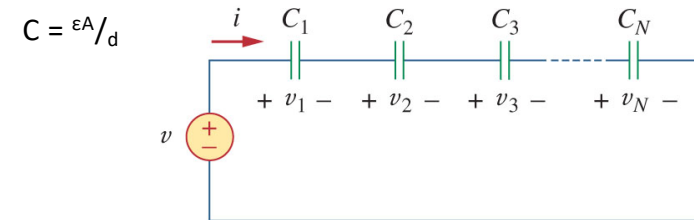

20

20

Inductors and Stored B

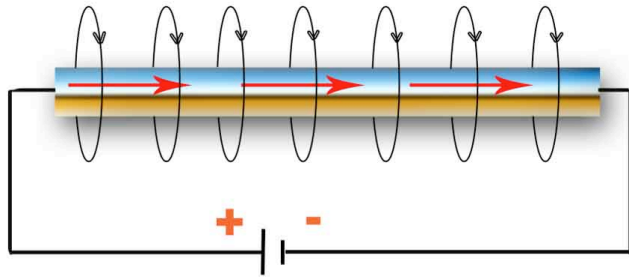

21

21

* Inductance *


- How is energy stored?
- Property of inductance – experimental observation:
 - A changing current (not a constant DC value)...
 - “induces” a _____
- V-I expression $v_L =$
- What are the restrictions on the current flowing through an inductor?
 - Think about calculus again
 - What is the steady-state behavior?



24

24


Inductors and Stored B

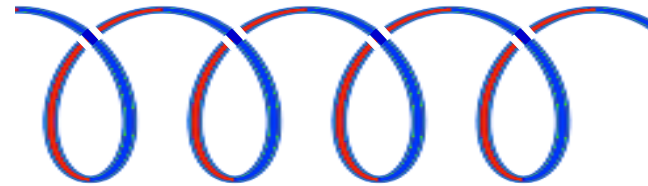

22

22


Equivalent Inductance

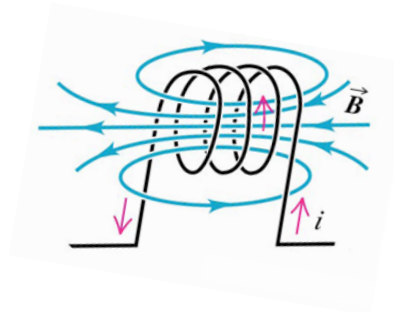

25


25

Equivalent Inductance

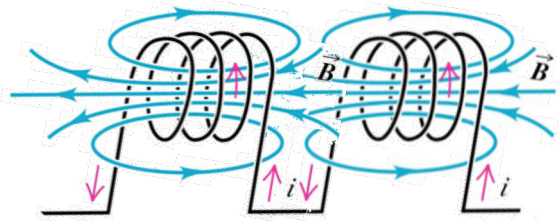


26

Series Inductors: L_{eq} ?

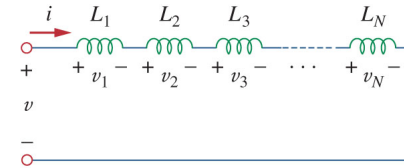

27

Parallel Inductors: L_{eq} ?

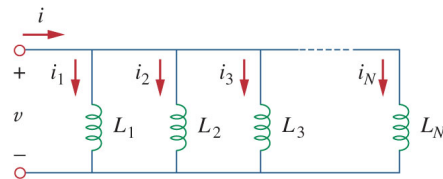


28

Natural Response + Steady-State of Dynamic Circuits


No initial stored energy, charging

Initial stored energy, discharging

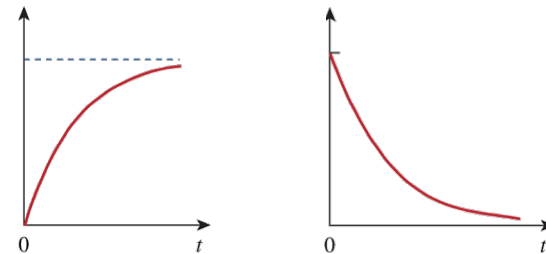

29

Next Lab: Explore “time constant”

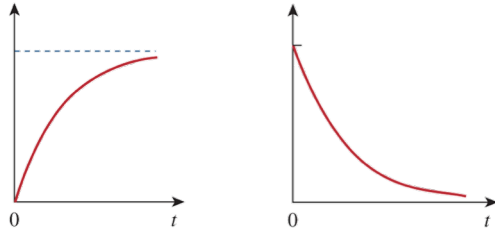

30


Capacitor & Inductor Concepts

- Know the $v-i$ relationship for
 - Resistors
 - Inductors
 - Capacitors
- Know the expressions for series and parallel
 - Resistors
 - Inductors
 - Capacitors



32

Next Lab: Explore “time constant” τ

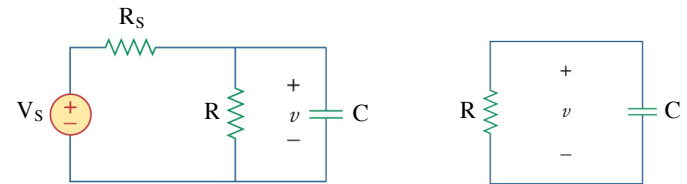

$$\tau = RC \quad (\text{Measured in seconds})$$



31

* Chapter 6 Recap *

- Capacitors and inductors, * **table 6.1** *
 - Definition and properties
 - Circuit analysis: $v-i$ relationship
 - Series and parallel combinations
 - Form of v and i are exponential (more in chapter 7)
 - When behavior is as a short or open circuit
- Physical, conservation laws
 - Know whether instantaneous changes in voltage and current are allowed or are impossible across/through elements



33



Questions?