



First Order Circuits I: Source-Free Circuits, the Natural Response

EGR 220, Chapter 7
March 3, 2020

1

Capacitors Review


- Stored charge, $Q =$
- V-I relationship: $i_c =$
- What does this tell us about the voltage across a capacitor?
 - Think about calculus and taking a derivative
 - What is the steady-state behavior?



3


Overview

 - First Order, Source-free circuits
 - One storage element = 1st order circuit
 - Source-free = Natural response
- Analysis method
 - Three time periods of interest
- Solution expression, $v(t)$ and $i(t)$
 - Time constant
- Examples
- Applets: <http://www.falstad.com/circuit/e-index.html>




2

Inductors and Stored B

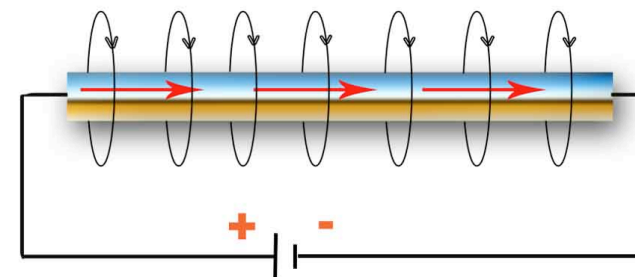

4

Inductors and Stored B

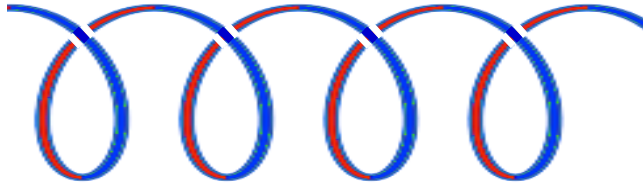

5


* Inductance *

- How is energy stored?
- Property of inductance – experimental observation:
 - A changing current (not a constant DC value)...
 - “induces” a _____
- V-I expression observed $v_L \sim$ _____ $v_L =$ _____
- Restrictions on current flowing through an inductor?
 - Think about calculus
 - What is the steady-state behavior?



7

Equivalent Inductance

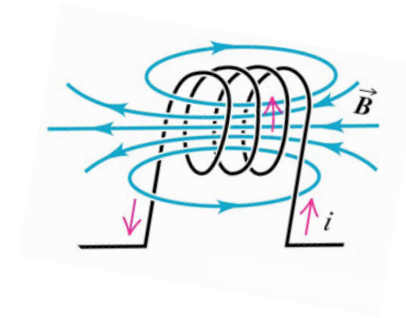

6


The ‘Constituent Relations’ for R, C and L

- (*i.e.*, What is the V-I relationship?)
- R: $V_R =$ _____; $I_R =$ _____
- C: $V_C =$ _____; $I_C =$ _____
- L: $V_L =$ _____; $I_L =$ _____
(the dual of the expression for C)



8


Equivalent Inductance

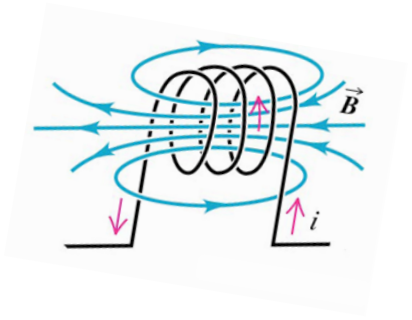

9

■ ■ ■ ■ ■ ■ ■


Equivalent Inductance

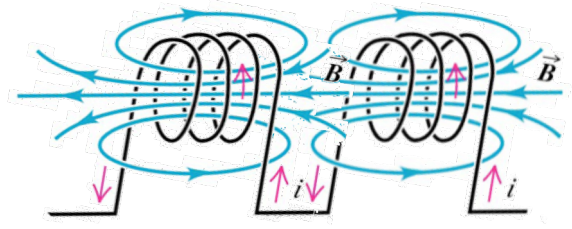

10

■ ■ ■ ■ ■ ■ ■


Series Inductors: L_{eq} ?

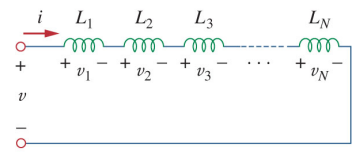

11

■ ■ ■ ■ ■ ■ ■

Parallel Inductors: L_{eq} ?

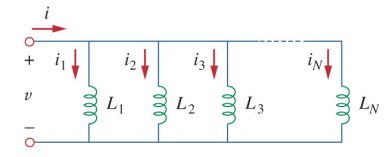


12


■ ■ ■ ■ ■ ■ ■

Natural Response of *First Order Circuit*

Charging

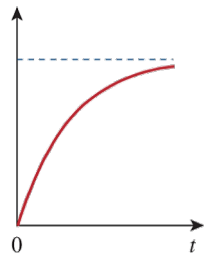


Discharging

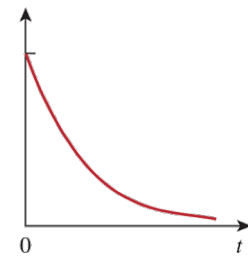

13


Charging and Discharging

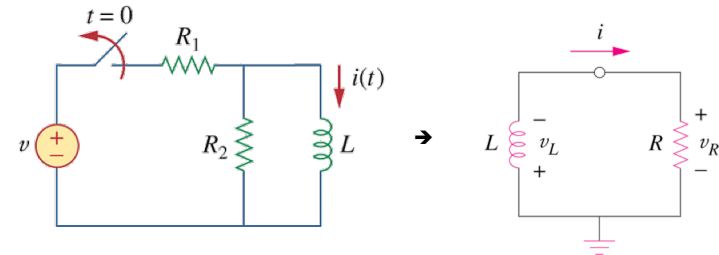

14

Steady-State Behavior

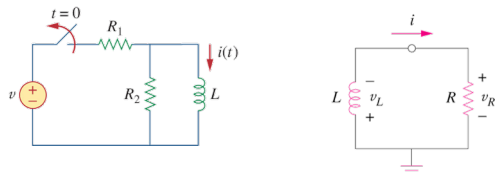- 1) The storage element charges, from a DC power supply
- 2) Steady-state behavior: After charging “for a long time,” the storage element becomes fully charged
 - “For a long time” is defined relative to the _____
- 3) The switch is opened and the power supply is disconnected
 - As time goes to infinity...



15

Steady-State Behavior

- After charging “for a long time,” the storage element becomes fully charged (typically the initial condition).
 - “For a long time” is defined relative to the _____
- Fully charged behavior is <open/short> circuit:
 - Capacitor: $i_C =$
Behaves as _____
 - Inductor: $v_L =$
Behaves as _____




16

Circuit Response

- **Natural response** → Initial stored energy
- **Forced response** → Power source connected
- **Complete response** → Initial stored energy + connected power source

Also called the 'step response'

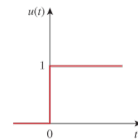


(No response at all → No initial stored energy and no power source)



17

Time periods of interest

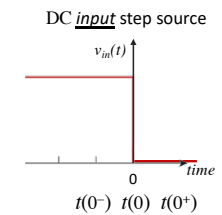
Steady-state 1 → transition → steady-state 2



1)

2)

3)

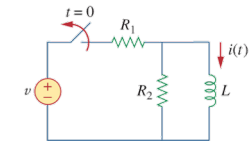

Assumptions:





18

Derive the Natural Response Expression

- Assumptions / **Initial conditions**
 - At $t = 0$, initial inductor current = _____?
 - At $t = 0$, R and L voltages are _____?
- Apply KVL in the loop, to find a mathematical expression for $i(t)$


KVL:

 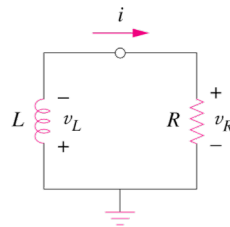


19

Derive the Natural Response Expression

- Show that $i(t) = I_0 e^{-tR/L}$

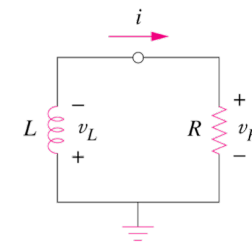

20

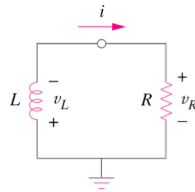


Derive the Natural Response Expression

- With the current equal to:

$$i(t) = I_0 e^{-tR/L} = I_0 e^{-t/\tau}$$

- How do we find $v_R(t)$ and $v_L(t)$?

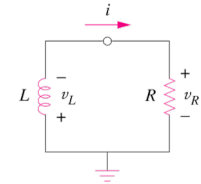

$$v_R(t) =$$

$$v_L(t) = -v_R(t) =$$

21

** Time Constant **

- Time constants for RC and RL circuits are defined as $\tau = RC$ and $\tau = L/R$
- A time constant is the time required for the response ($v(t)$ and $i(t)$) to decay by a factor of _____ of its initial value


$$v(t) = V_0 e^{-t/\tau}$$

$$i(t) = I_0 e^{-t/\tau}$$

24



22

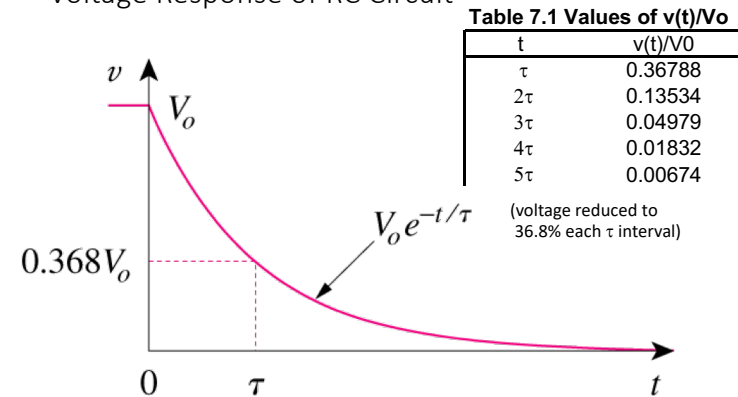Exponential Response:
Voltage Response of RC Circuit



25

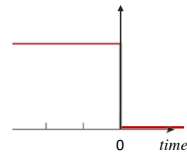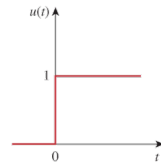
Switches: with Math and in a Circuit Diagram



26

RL Circuit

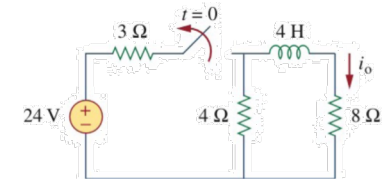
- Find $i(t)$
 - i_o for $t < 0$
 - τ for $t > 0$, with $R = R_{Th}$ at L



27

RL Circuit

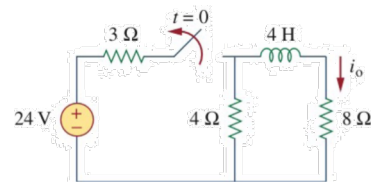
- Find $i(t)$
 - i_o for $t < 0$
 - τ for $t > 0$, with $R = R_{Th}$ at L



28

RL Circuit

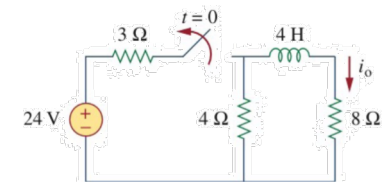
- Find $i(t)$
 - i_o for $t < 0$
 - τ for $t > 0$, with $R = R_{Th}$ at L



29

RC Circuit

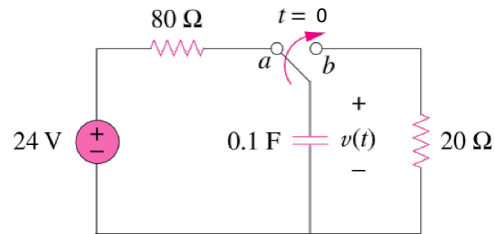
- At $t=0s$, the switch is moved from position a to b .
- **How** do we find $v_c(t)$, $i_c(t)$, $i_R(t)$, and $v_R(t)$ at $t=10s$




32

RC Circuit

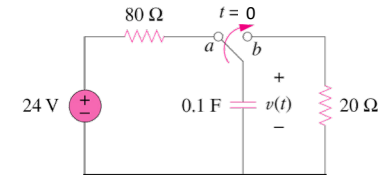- How do we find $v_c(t)$, $i_c(t)$, $i_R(t)$, and $v_R(t)$ at $t=10s$



33

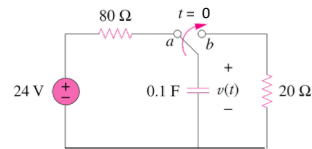

34

Lab this week ➤ Time Constants

- Chapter 7 – Use capacitors, not inductors, for lab
- Select R and C values for a time constant that you can use to watch and measure the capacitor charging.
 - Work on charging and then repeat with discharging.
 - Start with the DC power supply and multimeters, and then use the oscilloscope and function generator if you have time and experiments
- Experiment with capacitors
 - (In series with a resistor for equipment safety)
- Think of something you could time and use the RC circuit as a timer.
- Explore why exponential charging and decay explain all the natural dynamic behavior in the universe.



35



Time Constant





R =
C =
 τ =
bucket fills:

R =
C =
 τ =
bucket fills:



36

Explore "time constant" $\tau = RC$

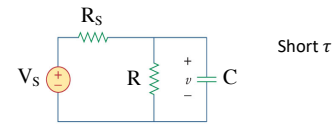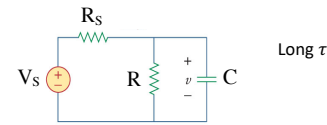

37

Lab Memo and Graphs

- Graphs and figures for the memo – read lab handout.
- Be sure to include, and explain, graphs of your circuit behavior in your lab memo.
 - If you will use the oscilloscope this week, then...
 - **Bring a USB drive**, save oscilloscope images and use the saved .png files in your memo
 - (If not this week, then definitely next week)



38

Self-Review: Interpret RL & RC Response

- Be comfortable with the answering the following
 - What is the time constant?
 - What is the graph of $i_L(t)$? Of $v_C(t)$
 - What are the graphs of $i_R(t)$, $v_R(t)$, $v_L(t)$ and $i_C(t)$?
 - What happens to the response as L changes?
 - ... As R changes? ... as C changes?
- Be comfortable finding power and energy for these circuits
 - What does the power represent? The energy?



39

Summary

- Source-free circuits
 - RC and RL circuits
 - Both are *first order* circuits
- Solving differential equations
 - Exponential and natural logs
- Natural response
- Time constant
- Step functions and switches



Questions?



40

41