



Circuit Topology & Kirchhoff's Laws

EGR 220, Chapter 2
Jan 30, 2020

Class Concepts

- Understanding circuit topology
 - Identifying nodes, branches & loops in circuits
- Open & Short circuits
 - Implied resistance for the branch
 - V across & I through for the branch
- Kirchhoff → Conservation laws
 - Current law, KCL (conservation of charge)
 - Voltage law, KVL (conservation of energy)



2

Recap: Electricity Concepts

- Define in words and with an equation/expression
- Current
 - Symbol and unit:
 -
- Resistance
 - Symbol and unit:
 -



4

Recap: Electricity Concepts

- Define in words and with an equation/expression
- Current
 - Symbol and unit:
 -
- Resistance
 - Symbol and unit:
 -
- Voltage
 - Symbol and unit:
 -
- Power
 - Symbol and unit:
 - How is power related to energy?



5

Defining a Circuit


- What elements can be in a circuit?
 - Energy source – independent and dependent
 - Energy dissipating element
 - Energy storage elements
 - A “load”
- Give examples of each element




6

Open & Short Circuits

Find
V & I for
resistors
 R_1 & R_2

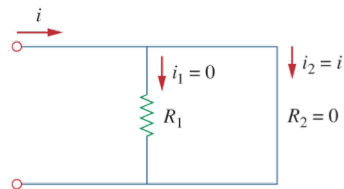

(a)

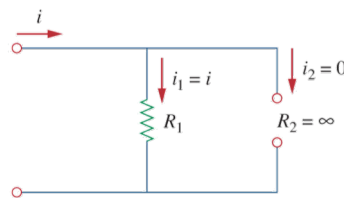

(b)



8

New Concepts: Open & Short Circuits

Tasks:

- Draw an example of each type of branch
- Relate each to Ohm’s Law ($V = IR$)
- What are V and I in each example?
 >(0? <0? >0? ∞ ?)



7

* Open & Short Circuits *

- If there is no current, can there be a voltage drop?
 - Examples?
- If there is no voltage drop, can there be current?
 - Examples?
- Power Sources
 - What is the difference between a current source and a voltage source?



9

New Concepts & Laws


- Node, Branch & Loop
- Series resistors
 - Series elements; series branches
 - Shared: nodes? current? voltage?
- Parallel resistors
 - Parallel elements; parallel branches
 - Shared: nodes? current? voltage?
- KVL: Kirchhoff's voltage law
- KCL: Kirchhoff's current law



10

Discuss: Nodes & Branches

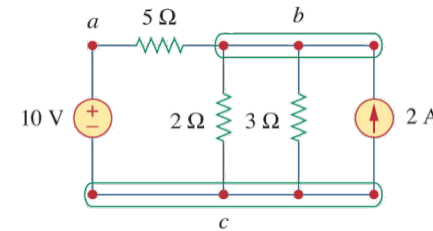
- A branch represents a single element such as a voltage source or a resistor.
- A node is the point of connection between two or more branches.



11


Identify nodes, branches & loops

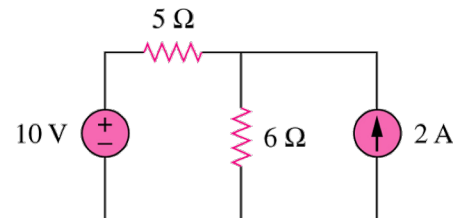- How many of each and where are they?
- Which elements are in parallel and which are in series?




12

Identify nodes, branches & loops; series and || elements

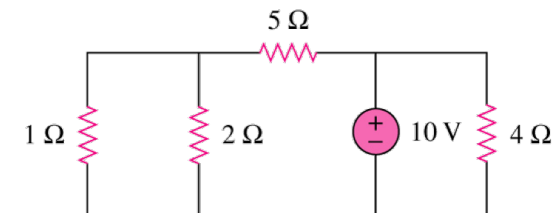


13

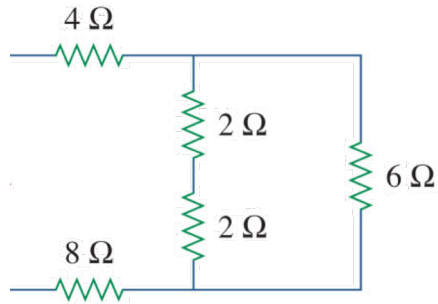Nodes, Branches, Loops, Series & Parallel



14

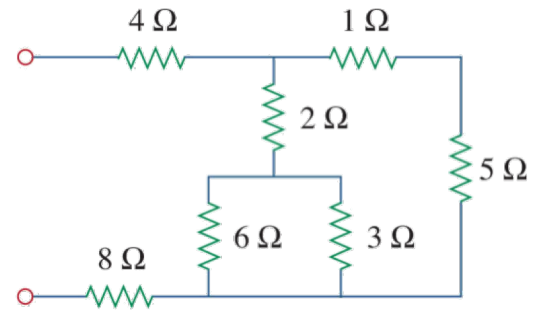Nodes, Branches, Loops, Series and Parallel



15


Kirchhoff's Current and Voltage Laws:
KVL & KCL



16

Kirchhoff's Current Law, KCL

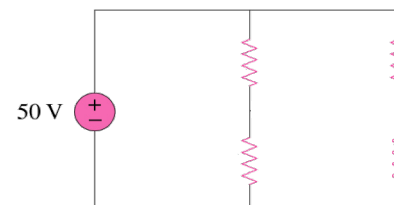
- Current flowing in = current flowing out.
- Principle of conservation of _____?
- The math expression is:



17


Kirchhoff's Current Law

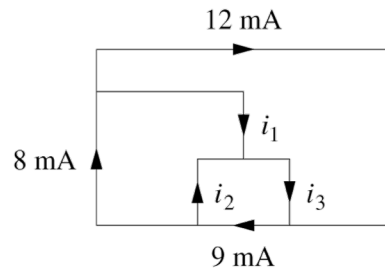- Find i_1 , i_2 and i_3
 - Label nodes
 - Write KCL eqn's
 - Solve
 - We will use Ohm's law when there are resistors in the circuit diagram



18


Kirchhoff's Current Law

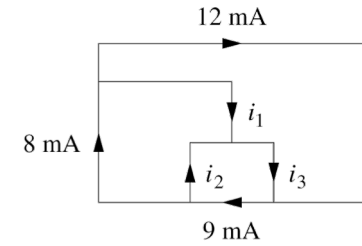

19


Kirchhoff's Voltage Law, KVL


For *EVERY* loop: $\sum V_{loop} = 0$

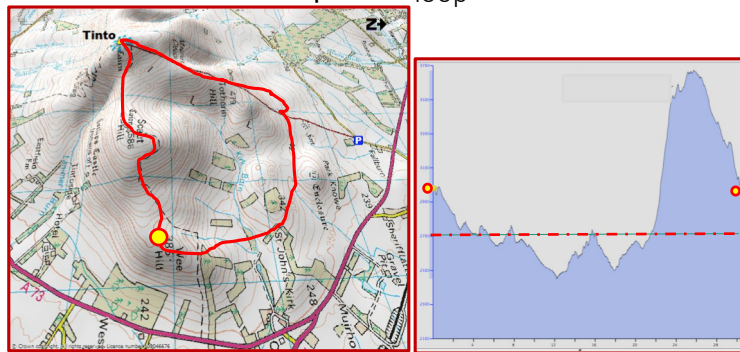

Kirchhoff's Voltage Law, KVL

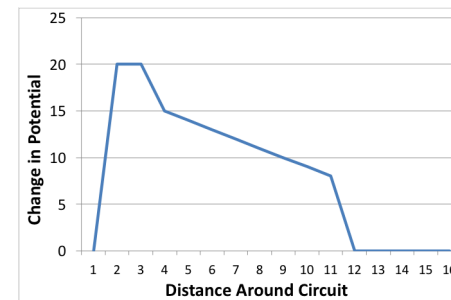
- Draw and label an electrical circuit that is consistent with the graph shown below.



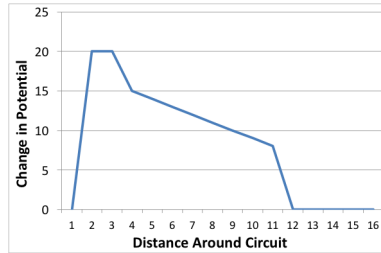


Kirchhoff's Voltage Law, KVL

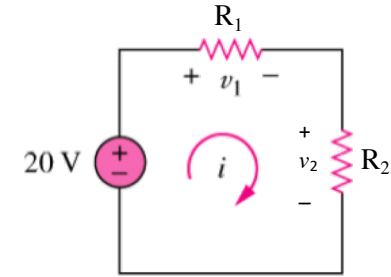- The conservation of _____
- Combine Ohm's law with KVL to solve for _____?



Kirchhoff's Voltage Law

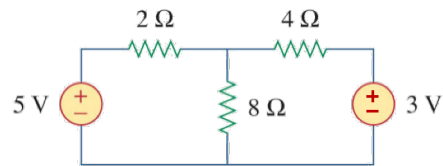- Apply KVL
 - Label voltages
 - Write KVL eqn's
 - We will solve later with mesh analysis



New Terminology

- Node
- Branch
- Loop
- Series
- Parallel



New Analysis Tools

- Ohm's law
- KVL: Kirchhoff's voltage law
- KCL: Kirchhoff's current law
- Current divider
- Voltage divider
- Equivalent resistance



26

Office & Tutor Hours

- Office Hours
 - Monday: 10:15 – 11:45
 - Tuesday: 1:30 – 2:30
- Master Tutor
 - Sunday – Thursday evenings there will always be 3 or so master tutors in the Playground
 - <https://www.smith.edu/glc/tutoring.html?colEGR=open#PanelEGR>
- Tani Somolu point person for EGR 220



27

Summary

- New Concepts
 - Kirchhoff's current and voltage laws
 - Series and parallel combinations
 - Open and short circuits
 - Nodes, branches and loops
- Labs
 - Pre-lab due **before** lab
 - One per team for 'design your own lab' days
 - Lab memo completed with partner, one memo per team



Questions?