



Kirchhoff's Laws II & Equivalent Resistance

EGR 220, Chapter 2
February 4, 2020

Class Concepts

- Open & short circuits
- Series and parallel elements
- Kirchhoff's Laws Examples
 - Current law, KCL
 - Voltage law, KVL
- Equivalent resistance
 - Series R_{eq}
 - Parallel R_{eq}



2

Open Circuits: V & I




3

Open Circuits: V & I



4

Homework Check-in

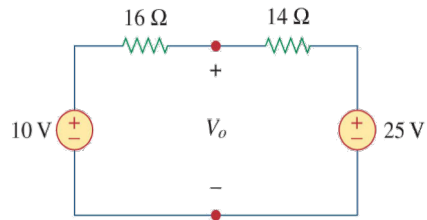

5


Recap: Node, Branch, Series and ||

- A **branch** represents a single element such as a voltage source or a resistor.
- A **node** is the point of connection between two or more branches.
- **Series** elements share a node **exclusively** (no third element shares the node)
- **Parallel** elements share the **same two nodes**



6

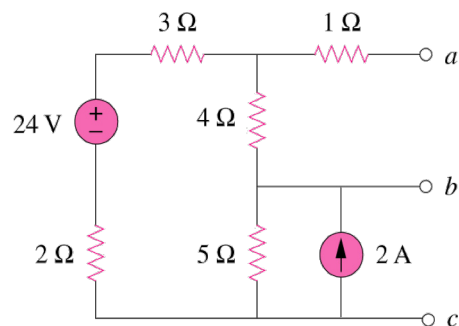
Series, Parallel, Open & Short and other things you notice



7


Kirchhoff's Current Law

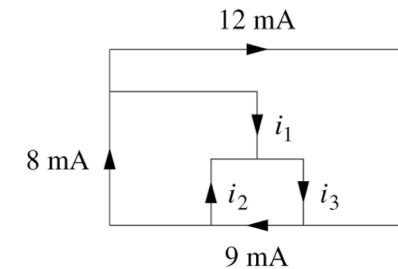- Find i_1 , i_2 and i_3
 - Label nodes
 - Write KCL eqn's
 - Solve
 - We will use Ohm's law when there are resistors in the circuit diagram



8


Kirchhoff's Current Law

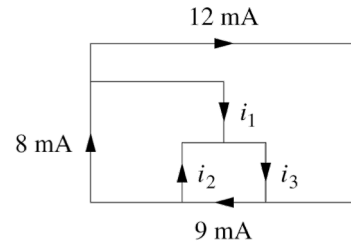


9

Kirchhoff's Current Law

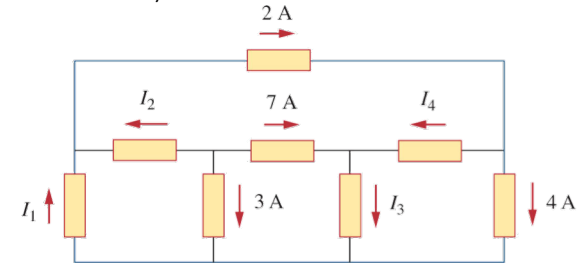- From HW 1: Find i_1 , i_2 , i_3 and i_4
 - Label nodes
 - Write KCL equation and solve (use Ohm's law for actual resistor circuits)




10

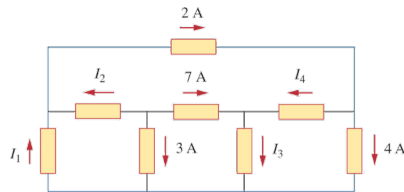


11

Kirchhoff's Voltage Law, KVL

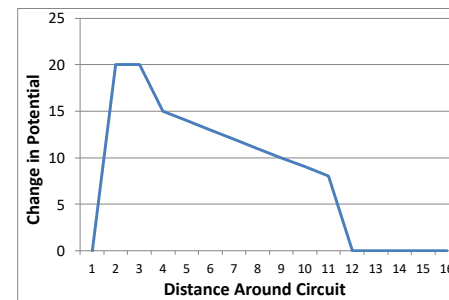
- Draw and label an electrical circuit that is consistent with the graph shown below.



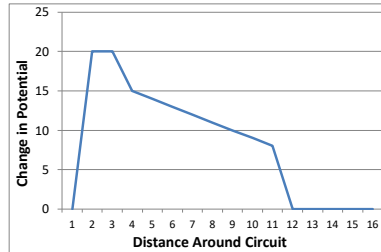


Kirchhoff's Voltage Law, KVL

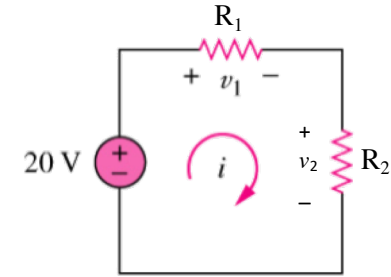- The conservation of _____
- Combine Ohm's law with KVL to solve for _____?



Kirchhoff's Voltage Law

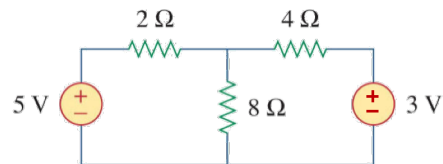- Apply KVL
 - Label voltages
 - Write KVL eqn's
 - We will solve later with mesh analysis



15


New Concept: Equivalent Resistance



16

Series Resistors

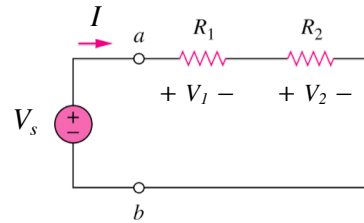
- Find R_{eq} (as a function of R_1 and R_2)




17

Parallel Resistors

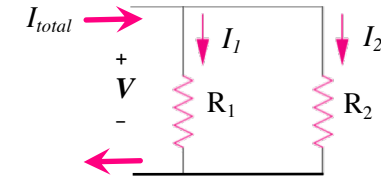
- Find R_{eq} (as a function of R_1 and R_2)



18

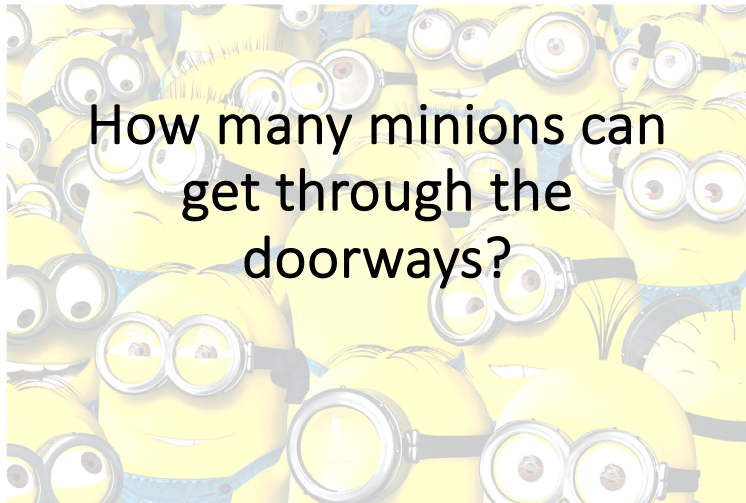


19

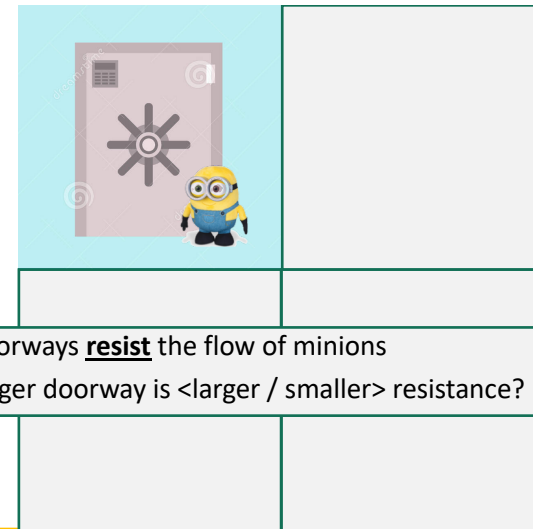


Download from
Dreamstime.com
18470211
Shutterstock | Dreamstime.com

20

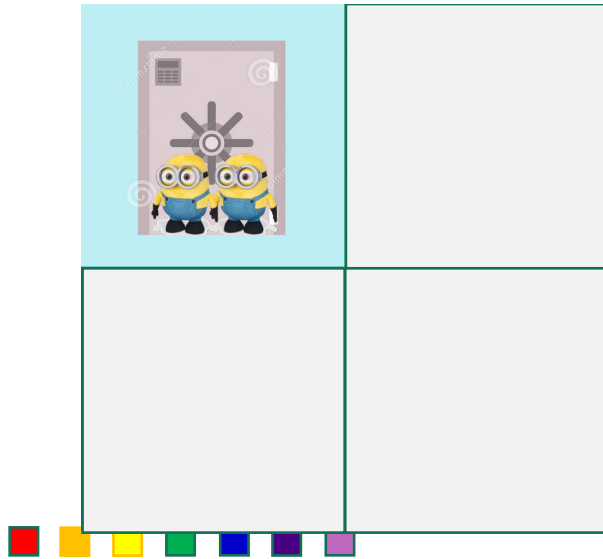

21

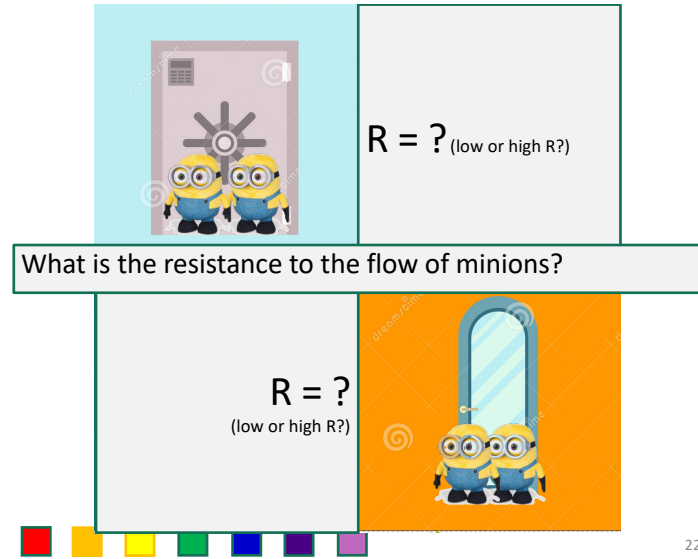

22



23

Resistance = 1 piece




24

Resistance = 2 pieces in series




25

Resistance Increasing

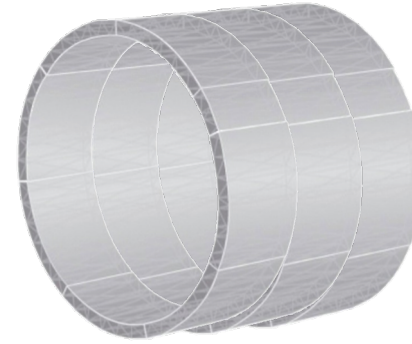

26

Resistance Increasing More

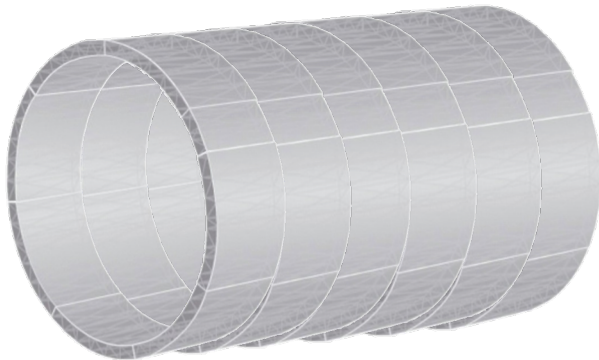

27


Equivalent Resistance

- Combinations of series and parallel resistors
- The same **current** flows through...
 - Series / parallel resistors?
 - (And the voltage across is divided)
- The same **voltage** drop is across..
 - Series / parallel resistors?
 - (Current through is divided)



28

Equivalent Resistance – Draw ...

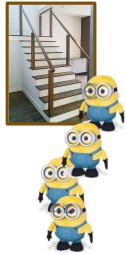

$$R = A\Omega$$

$$R = \frac{1}{2}A\Omega$$

$$R = 2A\Omega$$



29


Series & Parallel (text def)

- Two or more elements are in **series** if
 - They exclusively share a **single node** and
 - Carry the **same current**.
- Two or more elements are in **parallel** if
 - They are connected to the **same two nodes** and
 - Have the **same voltage across** them.




30

Identify Series and || Elements, and Find R_{eq}

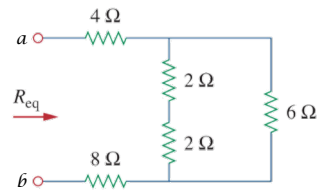


31

Identify Series and || Elements, and Find R_{eq}

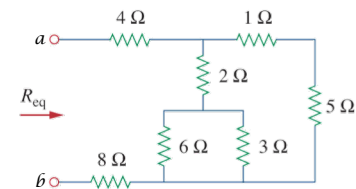


32

Identify Series and || Elements, and Find R_{eq}

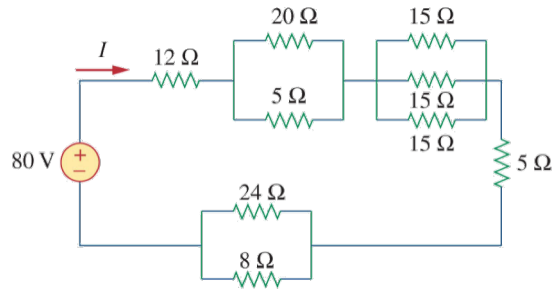


33

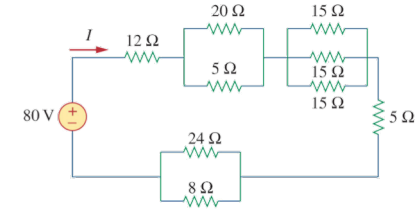

34

Different R_{eq} for Different Terminals

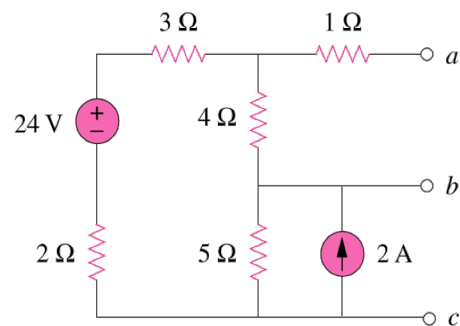

35

Equivalent Resistance

- Equivalent resistance is terminal-dependent


$$V_{\text{drop } a-b} = I_{a-b} * R_{eq}$$

$$R_{eq} = \frac{V_{\text{drop } a-b}}{I_{a-b}}$$


- *The ratio of voltage to current for **specific terminals** in a circuit*



36

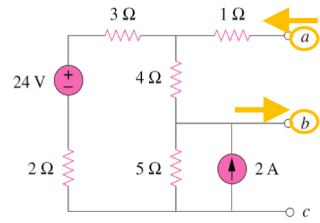

37

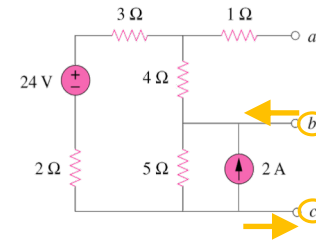

38

New Terminology

- Series elements
 - Share one node exclusively
 - Carry the same current
- Parallel elements
 - Share the same two nodes
 - Have the same voltage drop across
- Equivalent resistance
 - The ratio of voltage to current for the terminals (nodes) of interest



39



Questions?