



Voltage Divider Rule & Current Divider Rule

EGR 220, Chapter 2
Feb 6, 2020

Recap Concepts

- Series Elements (draw example)
 - **Exclusively share** a single node and
 - Carry the **same current**.
- Parallel Elements (draw example)
 - Share the same two nodes and
 - Have the same voltage drop across them.



3


Circuit Analysis Techniques

- Equivalent resistance, R_{eq}
 - Series and parallel resistors
- Current divider and voltage divider
- Mesh and nodal analysis
 - Building on KVL and KCL
- Review what we have done...
 - Bring questions to office hours



2


Find R_{eq} and I

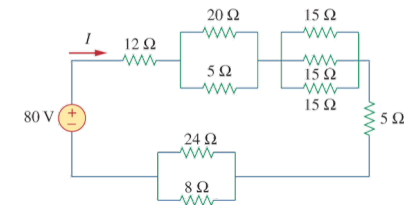


4

Different R_{eq} for Different Terminals

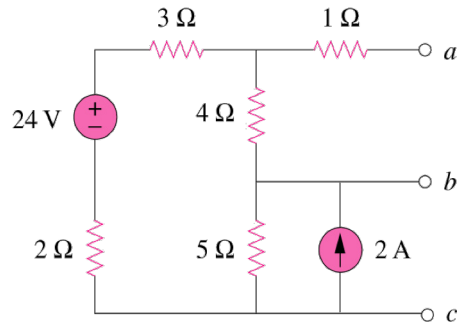
We will discuss the role of V_s and I_s later (with Thevenin equivalent)



5

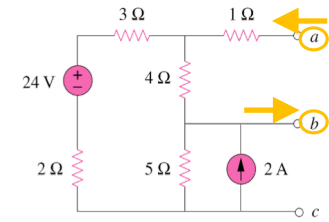


6

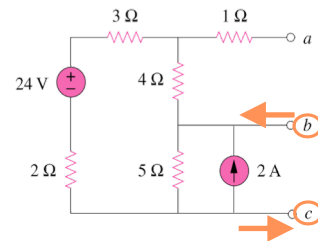

7

Voltage Divider Rule

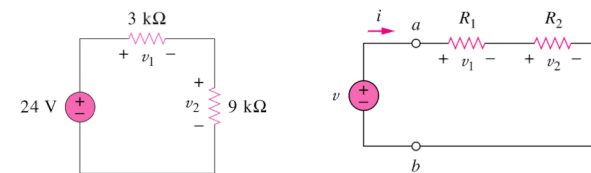
- **Resistors and elements in Series...**
- Current or voltage is the same for R_1 & R_2 ?
- Current or voltage is partitioned across R_1 & R_2 ?
- Prove, or demonstrate, using KCL and KVL.



8

Voltage Divider: Series R

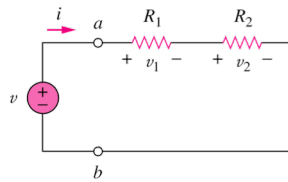
- Find v_1, v_2 in terms of v_{src}, R_1 & $R_2 \rightarrow$ derive the expression



9


Voltage Divider: Series R

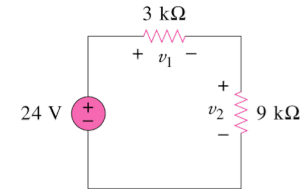- Solve for v_1 and v_2
 - Which resistor will have the larger V drop?



10


V-Divider Discussion

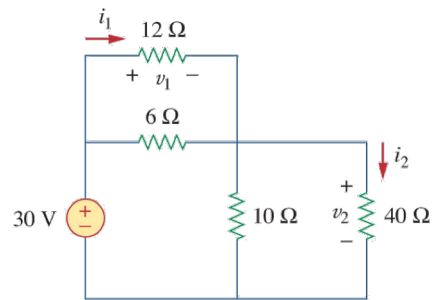

11

Current Divider Rule

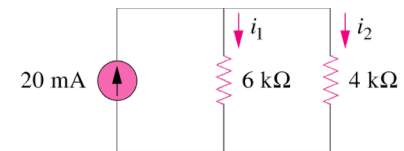
- Resistors, elements and branches in Parallel...**
- Current Divider:
 - I is partitioned, flowing through these resistors
 - What is the relationship of V for each element?
 - Prove, or demonstrate, using KCL and KVL.



12

Current Divider: Parallel R

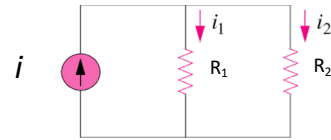
- Find i_1, i_2 in terms of i_{src}, R_1 & R_2
- Derive the expression...



13


Current Divider: Parallel R

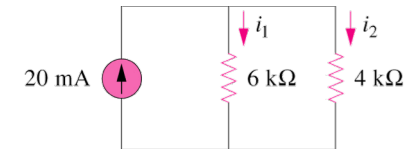- Solve for i_1 and i_2
 - Which R will carry the larger current?



14


I-Divider Discussion

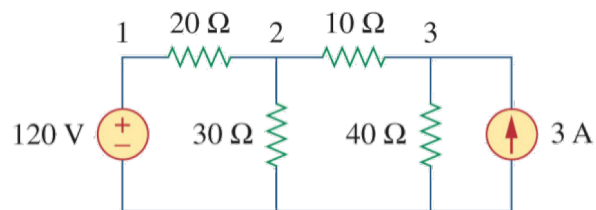

15

Lab Experiments – Find $R_{Multimeter}$

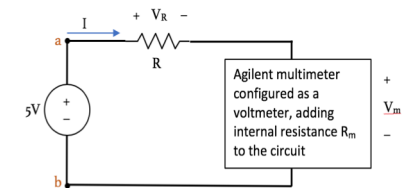
- (1) $R = 10M\Omega$
- (2) $R = 10k\Omega$



16

Lab Experiments – Find $R_{\text{Multimeter}}$


$R = 10\text{M}\Omega$

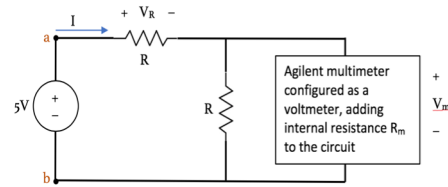

17

Lab Experiments – Find $R_{\text{Multimeter}}$


$R = 10\text{k}\Omega$

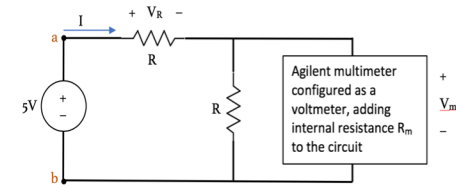

18


Ammeter – Introduced Error

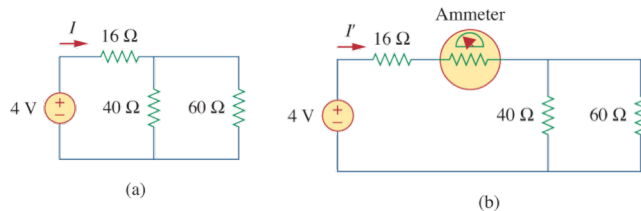- Find the current I in circuit (a).
- An ammeter with an internal resistance of 1Ω is inserted in the network to measure I as shown circuit (b). Does current, I , increase or decrease relative to part (a)?



19


Ammeter – Introduced Error

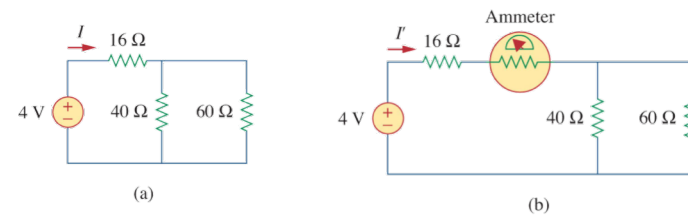

20


Voltmeter – Introduced Error

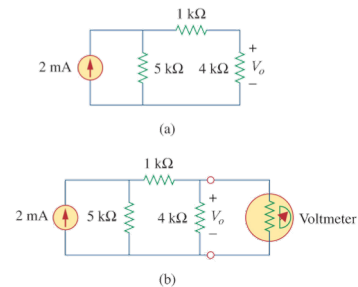- Calculate the voltage V_o in circuit (a).
- Is the voltage V_o , measured when a voltmeter with $6\text{-k}\Omega$ internal resistance is connected as in figure (b), greater or less than V_o in circuit (a)?



21

Voltmeter – Introduced Error

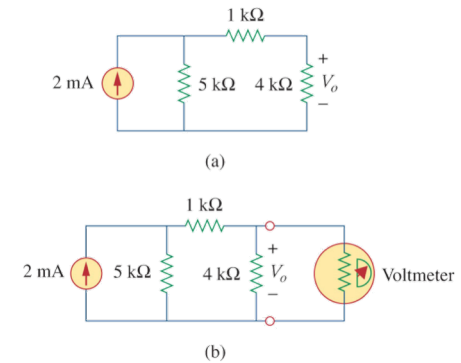

22

Fundamental Analysis Tools for the Semester

- Basic analysis laws
 - Ohm's law
 - KVL: Kirchhoff's voltage law
 - KCL: Kirchhoff's current law
- Analysis tools using the basic laws
 - Equivalent resistance
 - Current divider
 - Voltage divider
 - **Mesh analysis**
 - **Nodal analysis**
 - **Equivalent Circuits**



24



Questions?