



Mesh & Nodal Analysis

EGR 220, Chapter 3
Feb 11, 2020

Overview


- Use Ohm's Law, KVL & KCL for simultaneous equations with...
- Nodal Analysis
 - One equation per node
 - Solve for node voltages
- Mesh Analysis
 - One equation per loop
 - Solve for loop currents (not necessarily the same as element currents)



2

Recap Voltage Divider: Series R

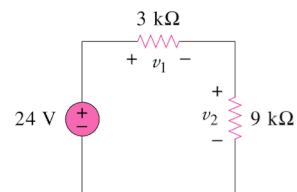
- Solve for v_1 and v_2
 - Think about which resistor will have the larger V drop



3



Recap Current Divider: Parallel R

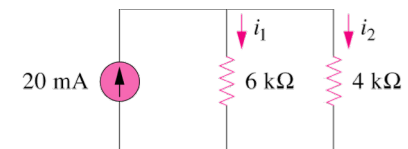- Solve for i_1 and i_2
 - Think about which R will carry the larger current





4

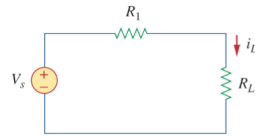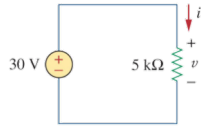Write Expressions for I , using Ohm's Law & "V_{drop}"



5

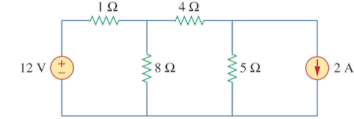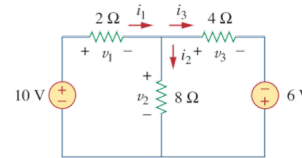Write Expressions for I , using Ohm's Law & "V_{drop}"



6

Nodal Analysis


- Apply Kirchhoff's current law to solve for nodal voltages
 - 1) **Label diagram** (nodes, all directions)
 - Initial labeling is arbitrary *but must be consistent!*
 - 2) **Obtain equations** using KCL and substituting in Ohm's law
 - 3) **Solve equations** for nodal voltages
 - Substitutions, linear algebra (matrices), Matlab
 - Note, negative answers indicate polarity is opposite your initial assumptions and are not incorrect
- Solution often requires **iteration**, as first attempt may not work.




9

Nodal Analysis

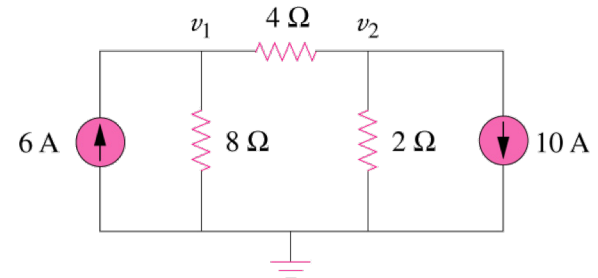
- How do we find v_1 , v_2 and power dissipated in the resistors?



10

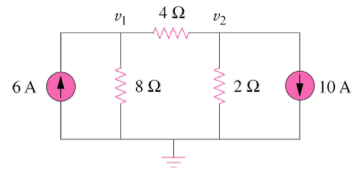


11

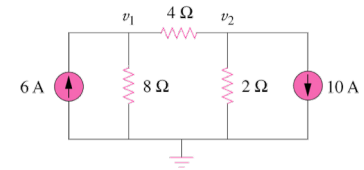

12

Concept Check: Voltage Across

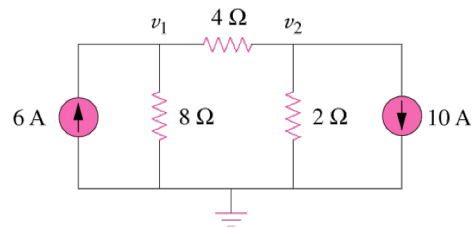- v_1, v_2 are voltage values relative to what?
- What is the voltage across the 4Ω resistor?



13

Mesh Analysis


- Apply Kirchhoff's voltage law to solve for loop (mesh) currents
 - Other law(s), expression(s) to use?
 - Process?
- 1)
 - 2)
 - 3)



14

Mesh Analysis Warmup

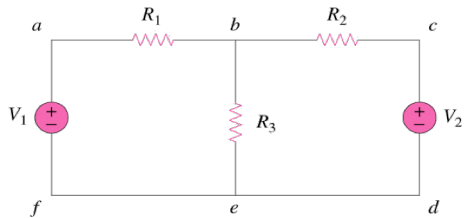
- How do we find (and label) i through R_3 ?
- Mesh currents versus element currents (linearity for resistor behavior; superposition of sources)



15

Mesh Analysis Warmup

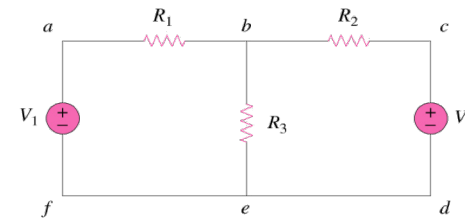
If we draw loop currents to be opposing through R_3 ...



16

Mesh Analysis

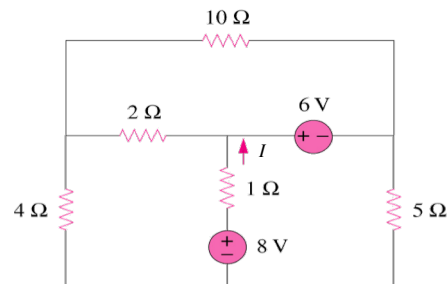
- How do we find I_1 , I_2 , I_3 and I ?
- Set up equations
- (be able to write equations in matrix format)



17

Mesh Analysis

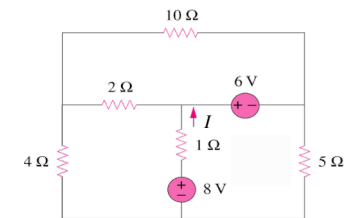
- Write equations for I_1 , I_2 , I_3 and I



18


Use Matlab to solve...
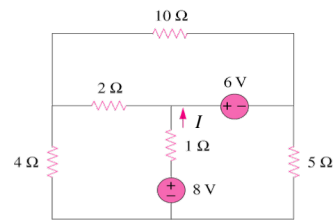
```
>> R = [7 2 1; 2 12 0; 1 0 6]
R = 7 2 1
    2 12 0
    1 0 6
>> V = [8; 6; 2]
V = 8
    6
    2
>> I = inv(R) * V
I = 1.0256
    0.3291
    0.1624
```



19


- Find all currents and voltages

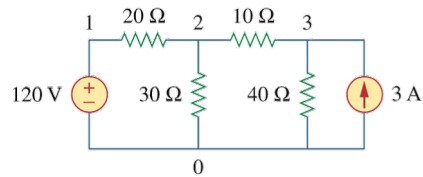

21

Practice Circuit Analysis 1


- Find all currents and voltages

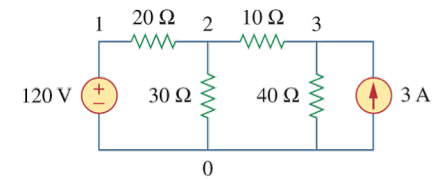

20


Discussion Circuit Analysis

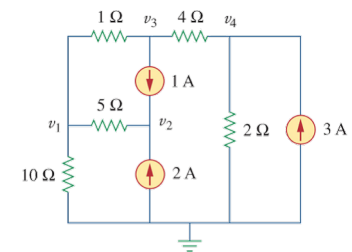- How can you find the voltages indicated?
- Compare ability to use nodal analysis vs. mesh analysis.



22


- How to find the voltages indicated?

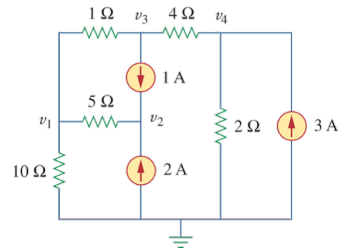

23


Practice Circuit Analysis 2

- Find all currents and voltages

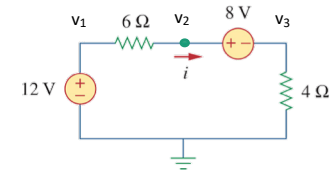


24

- Find all currents and voltages

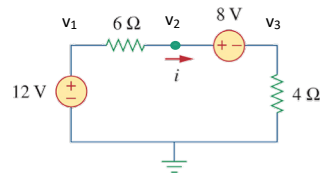


25

Practice Analysis

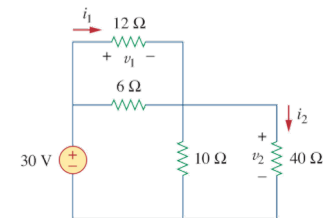

26


Practice Analysis

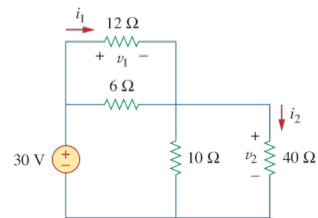


27

Practice Analysis (posted)

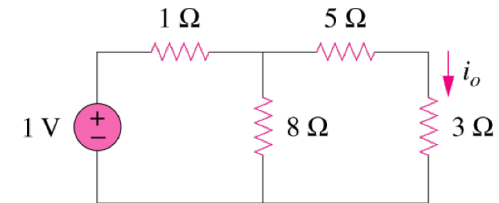- How would we apply the tools learned so far?
 - KCL → Nodal analysis
 - KVL → Mesh analysis
 - Current or voltage divider with R_{eq} ?



Practice Analysis

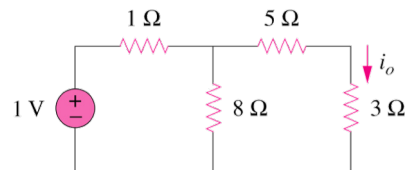

Analysis Tools

- Ohm's law
- KVL: Kirchhoff's voltage law
- KCL: Kirchhoff's current law
- Equivalent resistance
- Current divider
- Voltage divider
- Mesh analysis
- Nodal analysis
 - Exam 1 Through Mesh & Nodal ←
- Next core theorem: Thevenin Equivalent Circuit



30


Important Notes

- Read the text book!
 - We have limited in-class time
- Check out the applets link
 - on webpage from the first week of class
- Homework
 - show and develop clear thinking
 - *learn* from the homework




31

Lab 3: Linearity

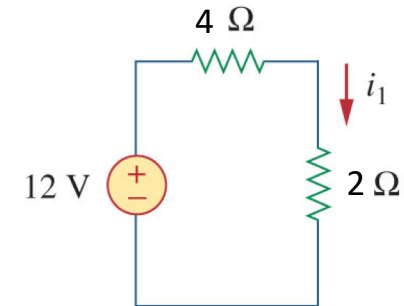

32

Lab 3: Superposition

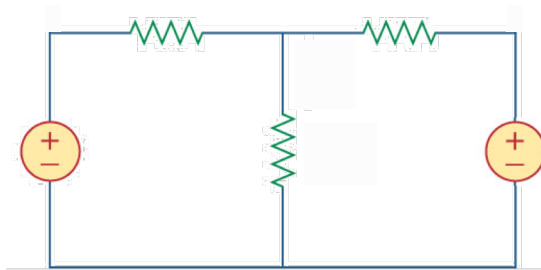

33

Lab 3 Preview


- **Design your own lab** – to verify Superposition and Linearity in circuits
- Read the chapter to begin learning these analysis methods
- Use **simple** circuits from the chapter to get ideas for your circuits, to build and test in the lab
- Pre-lab – design your lab experiment
 - **Design it for 1 ¼ hour**, allow time for mistakes and learning as you go, in our 2 ½ hour lab time.



34

Lab 2 Experiments – Find $R_{\text{Multimeter}}$


$R = 10\text{M}\Omega$

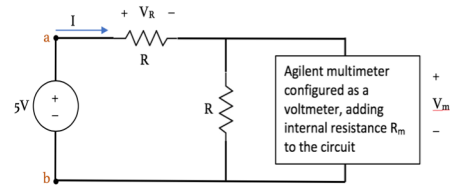

35

Lab 2 Experiments – Find $R_{\text{Multimeter}}$

$R = 10\text{k}\Omega$

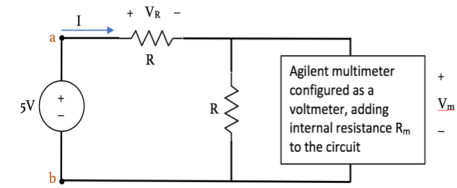

36