



Equivalent Circuits: Thevenin Theorem

EGR 220, Chapter 4.5 - 4.11
(not section 4.9)
February 20, 2020

1

Equivalent Resistance

- Equivalent resistance and voltage are terminal-dependent
- Ohm's Law tells us that $V = I \cdot R$ so...
 - $R = V/I$
 - Electrical resistance is the ratio of:
 - The (open circuit) voltage across a pair of nodes **to**
 - The (short circuit) through the pair of nodes



3

Overview

- Review concepts of
 - Voltage
 - R_{eq}
- **Thevenin Equivalent Circuit**
 - Equivalent V_s -with-series-R
 - "Equivalent" V-I-R behavior to an actual power supply or 'driving' circuit.



2

Equivalent circuits concept


- Indistinguishable from each other,
- ...In terms of the $V - I - R_{eq}$ characteristics,
- ...At the specified terminals (nodes)



4

Source Transformation & Equivalents

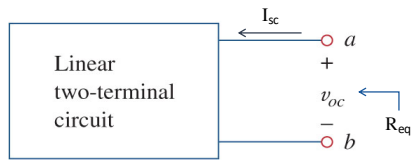- Voltage V_{ab} and R_{eq} can be measured across any nodes of **any** device or circuit.
- We are interested in this **measured orcalculated V – I – R behavior**



5 ("sc" = short circuit; "oc" = open circuit)

5


Your Mission

- Find two circuits with equivalent behavior with
 - 1) 1 current source + 1 resistor
 - 2) 1 voltage source + 1 resistor
- If you design a power source with output of
 - $I = \infty A \rightarrow$ Your computer will **melt**
 - $V = 0V \rightarrow$ Your computer will be a paper weight

7

7

Source Transformation


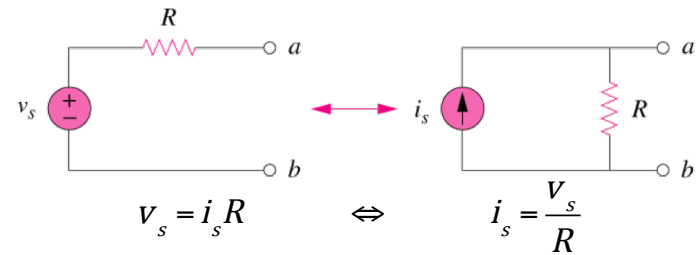


- Caution: maintain polarity of sources

6

6

Will your computer melt/do nothing?

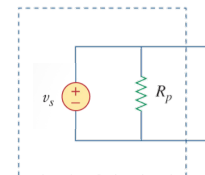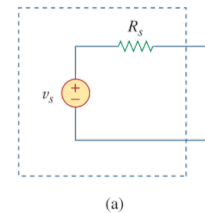


Find V_{oc} and I_{sc}


8

8

Will your computer melt/do nothing?

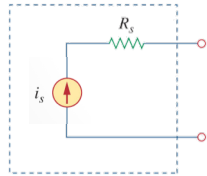


(a)

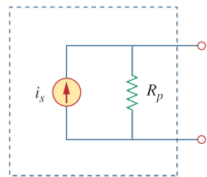


9

Find V_{oc} and I_{sc}

Later: Can these be equivalent?

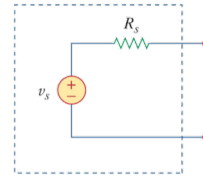


(a)

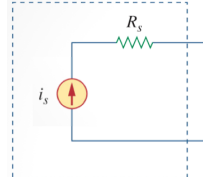


10

10

Later: Can these be equivalent?

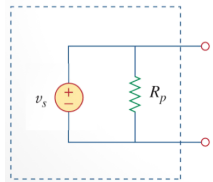


(a)

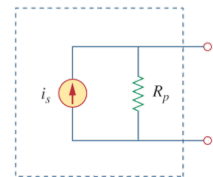


11

11

Later: Can these be equivalent?

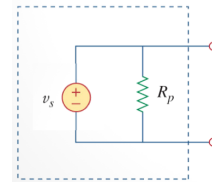

(a)

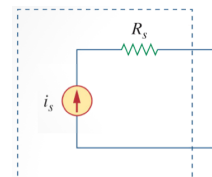


12

12


Source Transformation

- Find i in the circuit below

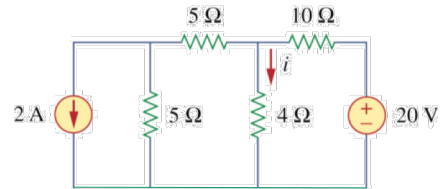


13

- Find i in the circuit below

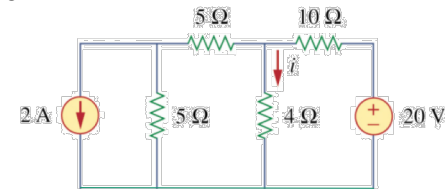

14


Thevenin Equivalent

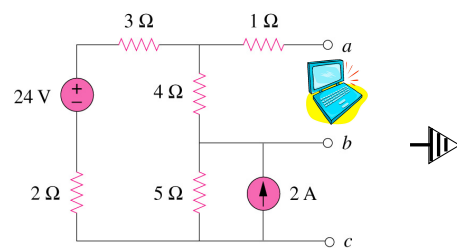



15

Thevenin Equivalent – Process

- Find R_{Th} :

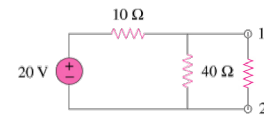

- Find V_{Th} :

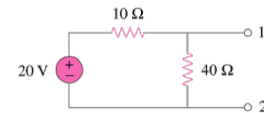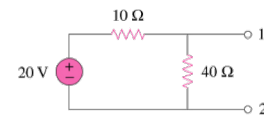


16

Thevenin Equivalent – Process

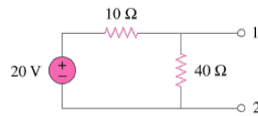1) Find R_{Th} :

- Remove the load resistor (**if there is one**)
- Set all (independent) sources equal to zero.
 - V-source = 0V \Rightarrow < open / short >
 - I-source = 0A \Rightarrow < open / short >
- Find the equivalent resistance from the specified nodes



17

17

Thevenin Equivalent – Process

1) Find R_{Th} :

- Remove the load resistor (if there is one)
- Set all (independent) sources equal to zero.
 - V-source = 0V \Rightarrow < open / short >
 - I-source = 0A \Rightarrow < open / short >
- Find the equivalent resistance from the specified nodes

2) Find V_{Th} :

- Return to the original circuit, remove the load again, but keep all sources, and
- Find the open-circuit voltage across the specified nodes



18

18

Thevenin Equivalent


- A Thevenin equivalent circuit is
 - An equivalent version of a different circuit
 - ...In terms of **the V-I characteristic, at the specified nodes**
 - Defined in terms of specified terminals/nodes
 - Consists of a single resistor, R_{Th} , and a voltage source, V_{Th}



19

19


Thevenin: Find V_{Th} , R_{Th}

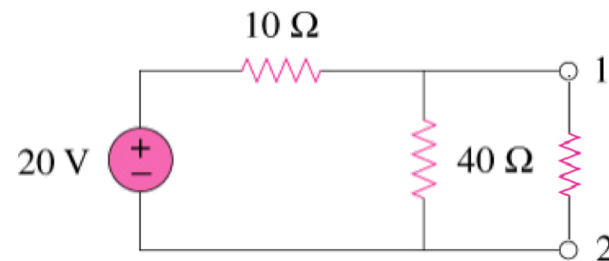


20

20


Thevenin: Find V_{Th} , R_{Th}

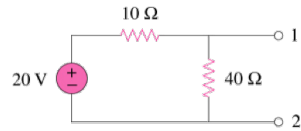


Thevenin: Find V_{Th} , R_{Th}

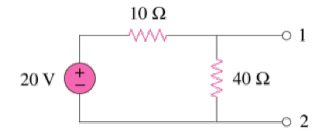


Thevenin: Find V_{Th} , R_{Th}

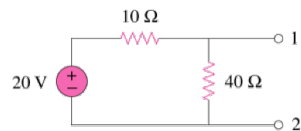

Thevenin: Find V_{Th} , R_{Th}

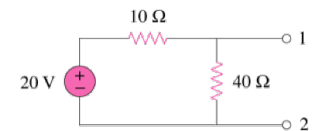


Thevenin: Find V_{Th} , R_{Th}

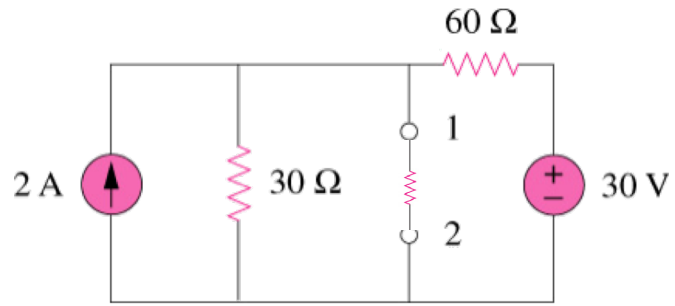

25

25

Thevenin: Find V_{Th} , R_{Th}

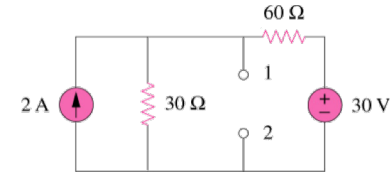


26

26

- Try setting up a solution method for all our analysis techniques and think about pros and cons of the different approaches


Thevenin: Find V_{Th} , R_{Th}

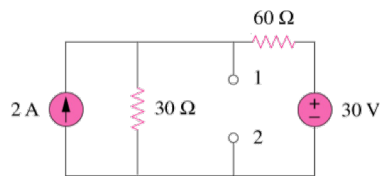

27

27


Thevenin: Find V_{Th} , R_{Th}

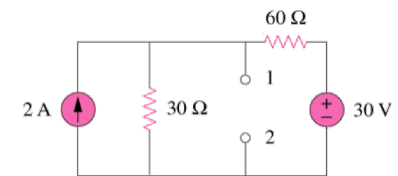

28


28

Thevenin: Find V_{Th} , R_{Th}

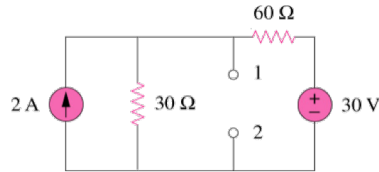

29


Thevenin: Find V_{Th} , R_{Th}

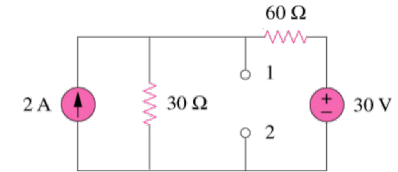

30

* Maximum Power Transfer *

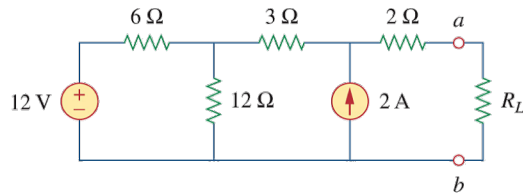
- **How** would we find the P_{max} delivered to R_L ?
- Do not solve – discuss strategy (chapter example)



31

Concept Question

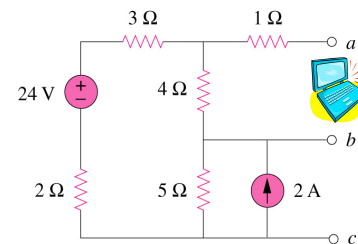
- Are equivalent circuits all the same?
- Discuss V_{Th} , R_{Th} at $a-b$ and $b-c$
- What is R_L for maximum power transfer, and how do you find the amount of power transferred?



32

Concept Question

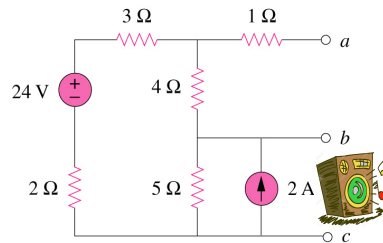- Are equivalent circuits all the same?
- Discuss V_{Th} , R_{Th} at a - b and b - c
- What is R_L for maximum power transfer, and how do you find the amount of power transferred?



33

33

Thevenin Self-Review

- What is a Thevenin Equivalent Circuit?
 - Draw a generic Thevenin equivalent circuit
 - Discuss and write down 3 good uses for a Thevenin equivalent circuit, or for the Thevenin theorem
- How might you find the maximum power that can be delivered to any load from any circuit?
 - Why is this an important question?



34

34

Norton Equivalent Circuit

$$V_{Th} = v_{oc}$$

$$I_N = i_{sc}$$

$$R_{Th} = R_N = R_{in} = \frac{v_{oc}}{i_{sc}}$$



35

35

Summary

- Source transformation
- Equivalency
 - Equivalent resistance
 - Voltage – Current – R_{eq} behavior
- Thevenin equivalent circuit
 - V-source & series resistor
 - Uses for Thevenin equivalent circuits
 - Only need to know the Norton equivalent exists. We will focus on Thevenin



36

36



Questions?