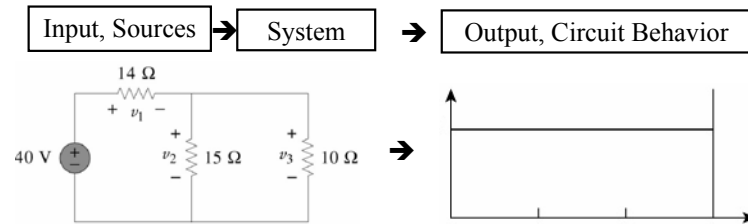


Second Order Circuits I: Initial Conditions

EGR 220, Chapter 8.1 – 8.2

October 9, 2005


Concept Map 3




➤ DC, static circuits: Chapters 1 through 4

2

Concept Map 3

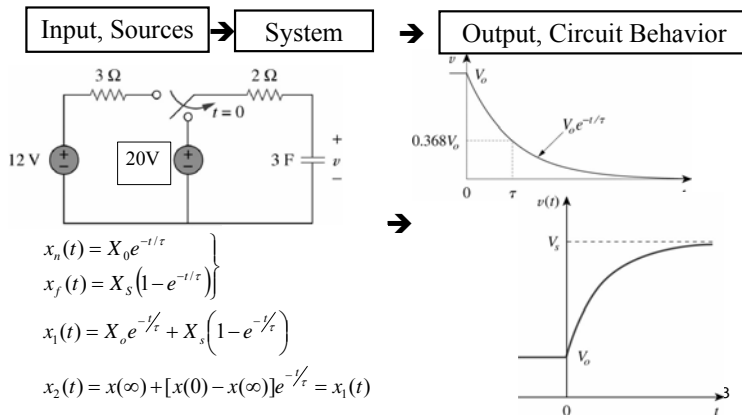

Concept Map 3

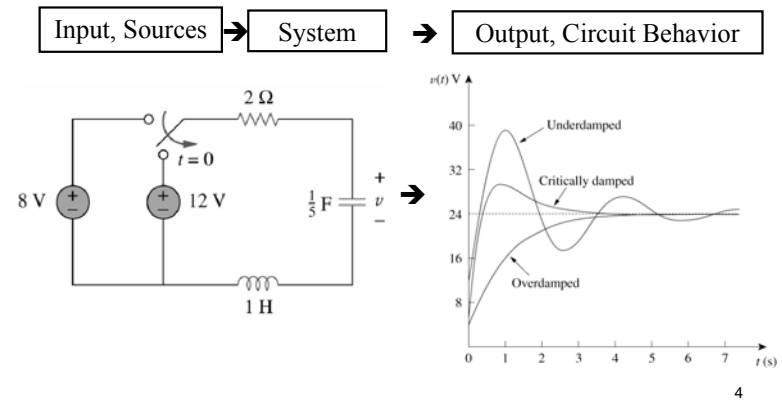

4

Overview

- Review of first order circuit solutions
- * Initial values for second order circuits *
- Circuit solutions
 - Source-free response – Today
 - Complete response – Next Thursday
- Damping of circuit response – next class

5


Recap: Step Response of RC & RL Circuits

- The step response is the complete response
- The complete (total) response is the sum of
 - The natural + the forced response
 - The transient + the steady state response
- Circuits may have a variety of inputs
 - Step input
 - (Sinusoidal input – next chapters)
 - (Ramp input; impulse (delta) input – EGR 320)

6

Recap: Step Response of an RC Circuit

- Find $v(t)$ (prob. 7.40)

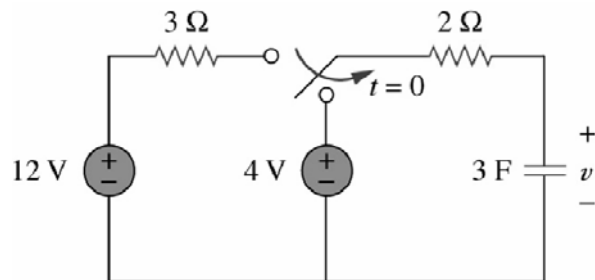

7

Recap: Step Response of an RC Circuit

- Three solution methods
 - Use *superposition* of natural response and forced response
 - Use text equation, applicable for the step response
 - (Use *transient* and *steady-state* response)
- Be comfortable with what every term in each solution method represents

8

Second Order Circuit Analysis

- “Second order circuits” means what?
 - Second order differential equations are required to describe the behavior of RLC circuits
 - Contain _____ storage elements?
- What do we want to discover through analyzing the circuit?
- What time periods are of interest?
- What initial information do we need?
- How do we proceed with the analysis?

9


Second Order Circuit Analysis

- How we begin to find initial conditions
 - Focus on the variables that cannot change instantaneously, which are...
 - Capacitor (voltage/current) _____
 - Inductor (voltage/current) _____
- For a second order circuit, we need values for two initial conditions (two constants of integration)
 - (We also find the final values at $t = \infty$)

10

Initial Values (problem 8.2)

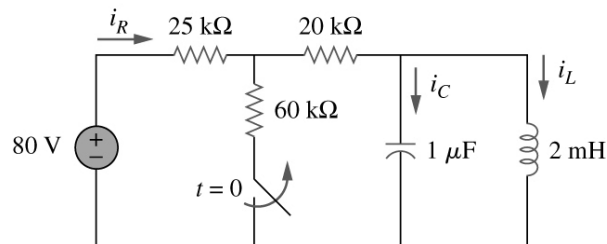
- Find: $i_R(0^+)$, $i_L(0^+)$ and $i_C(0^+)$,
- and: $di_R(0^+)/dt$, $di_L(0^+)/dt$ and $di_C(0^+)/dt$,
- and: $i_R(\infty)$, $i_L(\infty)$ and $i_C(\infty)$



11


Initial Values 1

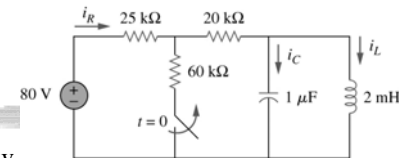1. Write down everything we know about the circuit



12


Initial Values 1

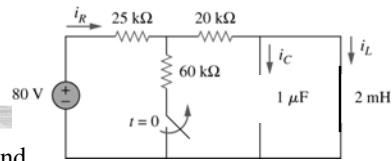

2. Begin solving: For time $t = 0^-$ find
 $\Rightarrow i_L(0^-)$ and
 $\Rightarrow v_c(0^-)$ (Which also tell us what?)

13


Initial Values 1

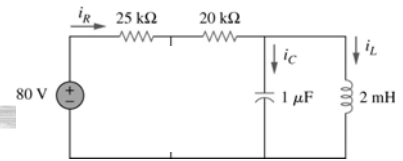

3. For time $t = 0^+$, find
 $\Rightarrow i_R(0^+)$ (use KVL) and
 $\Rightarrow i_c(0^+)$ (use KCL)

14


Initial Values 1

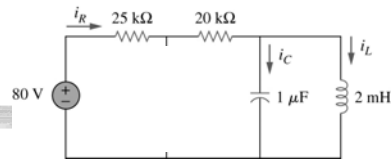

4. Now find the first derivatives:
 What do we know about $v_L(t)$ in general, and what can we deduce about $v_L(0^+)$?
 Use this to find $di_L(0^+)/dt$

15


Initial Values 1

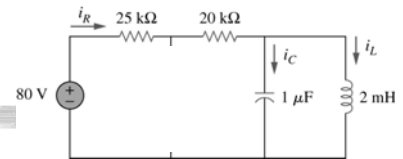

5. Finding $di_R(0^+)/dt$
 \Rightarrow Use ' $d(\text{KVL})/dt$ ' to find an expression for $di_R(0^+)/dt$
 \Rightarrow Use $i_c = C(dv_c/dt)$ to solve for $di_R(0^+)/dt$

16


Initial Values 1

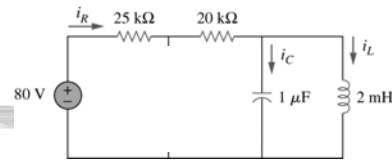

6. Finally, find $di_C(0^+)/dt$
⇒ Use 'd(KCL)/dt' to find an expression for $di_C(0^+)/dt$

17

Initial Values 1

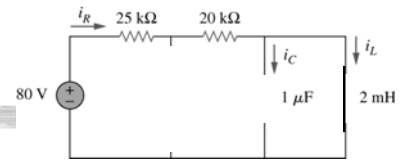

7. Find the final values, at $t = \infty$
⇒ $i_L(\infty) =$
⇒ $i_R(\infty) =$
⇒ $i_C(\infty) =$

18

Next Class: Circuit Response & Damping

- What are the three categories of damped response?
- What is being damped?
- What is doing the damping?
- What affects the type of damping?

19

Summary

- Second order circuits
 - Solving second order differential equations
 - Understanding energy storage and oscillatory circuit response
- Damping
 - Over-, critically and under-damped response

20