

Second Order Circuits III

EGR 220, Sections 8.5 – 8.7
October 27, 2009

Overview

- Second order circuits complete response
 - Natural response, *plus*
 - Forced response
- General RLC circuits
 - Develop the second order diff-eq. to solve for $i(t)$ or $v(t)$

2

Homework 8 Comments

- Finding $v(t)$ from $i(t)$ (8.17)
 - Integrate and include the initial condition as needed
- Using the differential equation to solve for $v(t)$ or $i(t)$
 - Using coefficients to find R, L, C and source

3

Terminology Review

- Define and describe how we find:
 - Characteristic equation $s^2 + \frac{R}{L}s + \frac{1}{LC}$ (series)
 - Natural frequencies $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$
 - Resonant frequency $\omega_0 = \frac{1}{\sqrt{LC}}$
 - Damping factor $\alpha = \frac{R}{2L}$ (series) $= \frac{1}{2RC}$ (parallel)
 - Damping frequency – for underdamped systems

4

2nd Order Circuit Analysis

1. Determine the type of damping (in order to know the form of the solution)
 - Write the general form of the solution, to use as you continue
2. Start finding the initial conditions
 - Decide which initial conditions are easiest to find, and do so
3. Find the natural or transient response
 - ⇒ Find the natural frequencies
4. Find the forced response, $x_f(t) = x_f(\infty)$
 - ⇒ Set up the solution with s_1 and s_2 substituted in, leaving the constants unknown
5. Solve for the constants, using the initial conditions
6. Check that your solution makes sense

5

Recap: Solution Format


$$x(t) = X_f + X_n$$

$$x(t) = X_f + A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

6

Step Response of Parallel RLC Circuit


- Find $v(t)$ for $t > 0$?

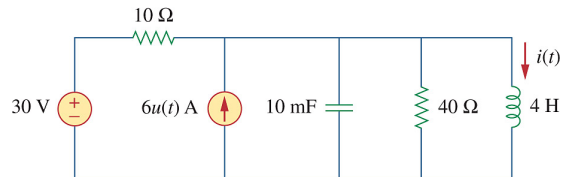

7

General Second Order Circuit

- Find $i(t)$ and $v(t)$ for $t \geq 0$

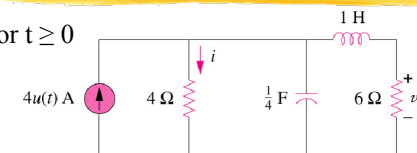

8

Summary

- Step response of
 - Parallel RLC circuits (KCL)
 - Series RLC circuits (KVL)
- General solution approach for second order circuits

9

Office Hours

- Tuesday
 - 2:30 – 3:30
- Wednesday
 - Lunch

10