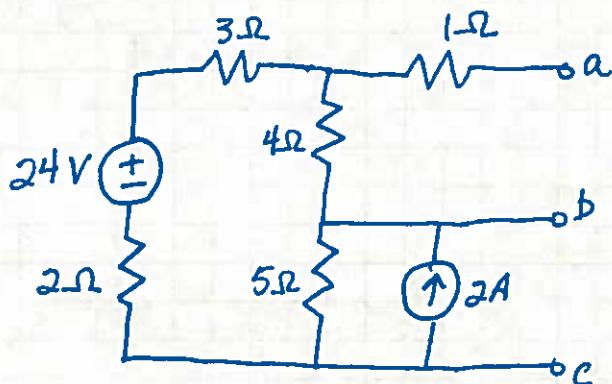


Class Problem- Thevenin Equivalent Circuits

(1)

Obj → to demonstrate that the Thevenin equivalent circuit is dependant upon which terminals, or nodes, you specify as the output nodes

Circuit




(a) Specifying terminals a-b as the output terminals

This means that "b" is the ground, or 0V node, in this situation.

Find R_{TH} • zero out sources

• find R_{eq} from "a" to "b"

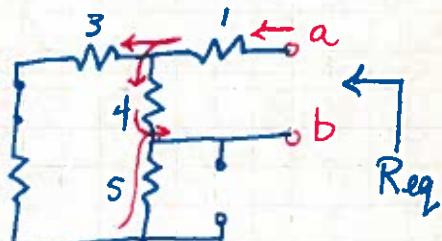

R_{eq} starting at node "a", flowing around through all branches and coming back together to flow out "b"

$$we \ set \ R_{eq} = 1 + (3+2+5) \parallel 4 = 1 + 10 \parallel 4 = 1 + 2.86 = \boxed{3.86 \Omega}$$

Find V_{TH} • replace all sources, to return to original circuit

• identify which voltage = V_{TH}

• find that voltage using all / any circuit analysis technique that is useful.

(Thermin example)

(2)

- As required for this method (finding a Thermin equivalent circuit), you must have an open circuit across the specified output terminals ("a"- "b" for now)
- This means no current flows at the output terminals
- So, for this example no current flows through the 1Ω resistor
- Therefore there is no voltage difference across the $1\Omega R$
- So, $V_{Th} = V_{a,b} = V_{\text{across the } 4\Omega R}$

Finding V_{Th}


Using mesh analysis

KVL:

$$2I_1 - 24 + 3I_1 + 4I_1 + 5(I_1 + I_2) = 0$$

$$14I_1 - 24 + 10 = 0$$

$$14I_1 = 14 \text{ so } I_1 = 1A$$

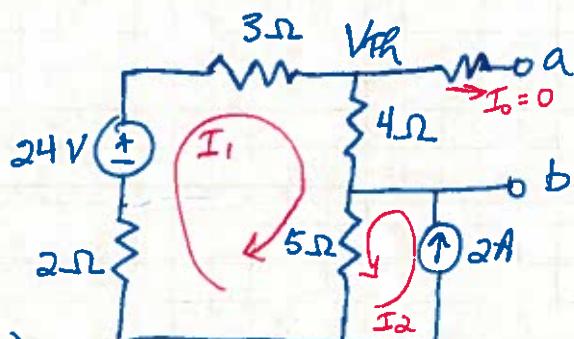


note $I_2 = 2A$

Ohm's law for the $4\Omega R$, which shares our output nodes (since $I_0 = 0$)

$$V_{Th} = IR = (1A)(4\Omega) = 4V$$


* Final thermin equivalent circuit *

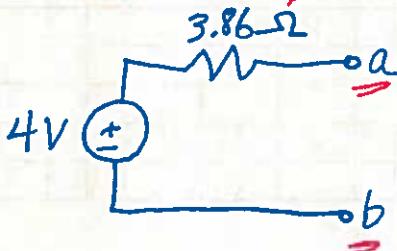

This means a load connected to terminals "a-b" above, or to the equivalent at left will not be able to distinguish between them

b) Thevenin equivalent for terminals b-c

(3)

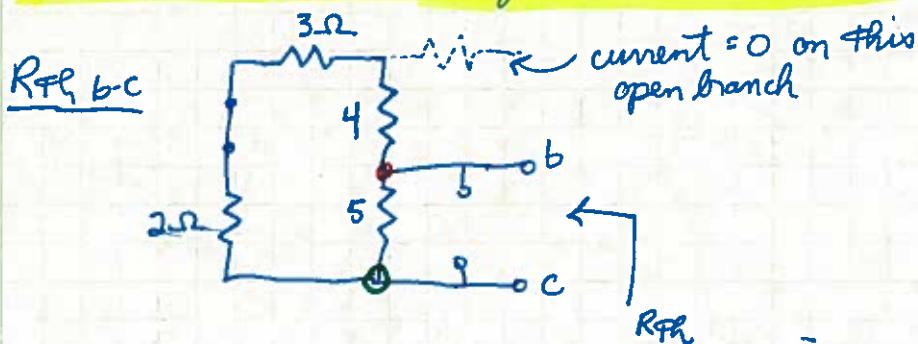


Being an electron that is traveling from "b" to "c" you would immediately encounter a branching or forking path, at the red dot. Hmm, to go through the 4Ω resistor or the 5Ω resistor? But wait, the $4\Omega R$ is in series with a $3\Omega + 2\Omega R$, so in fact the decision is between a $5\Omega R$ and an equivalent of $(4+3+2)\Omega R$.

Flowing along these two branches, you would find they come back together at the common node with the green circle. These branches share 2 nodes: \bullet $\$$ \circ

This means the $5\Omega R$ is in parallel with $(4+3+2)\Omega$ branch

$$R_{Th} = R_{eq} = \left(\frac{1}{5} + \frac{1}{4+3+2} \right)^{-1} = 3.2\Omega$$

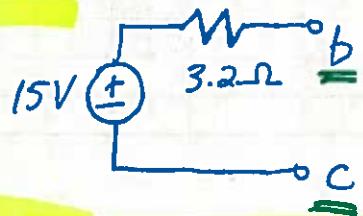$V_{Th\ b-c}$. The circuit analysis is the same as for $V_{Th\ a-b}$, except now you need to identify which voltage drop = $V_{Th\ b-c}$. This is the same as the voltage across the $5\Omega R$ or the $2A$ source. Using Ohm's Law for the 5Ω Resistor we find $V_{Th} = IR = (I_1 + I_2)5 = (1+2)5 = 15V$



\neq Thevenin equivalent
for terminals a-b.