

Review of AC Circuits & First Look at a Transmission System

Smith College, EGR 325
March 25, 2008

1

Objectives

- Know EGR 220 concepts
 - Power calculations and terminology
- Expand understanding of electrical power
 - from simple linear circuits to
 - a high voltage power system

2

Review (on own) Objectives

- EGR 220
 - Sinusoidal waveform representation
 - Root mean square
 - Phase shift
 - Phasors
 - Complex numbers
 - Complex impedance
- Electric Power
 - Complex: real & reactive power
 - Power factor and power factor correction

3

Objectives

- E-M energy storage
 - Capacitance & inductance
- Power calculations and terminology
- Expand understanding of electrical power
 - from simple linear circuits to
 - a high voltage power system

4

Dynamic Circuit Elements

- What does 'dynamic' mean (versus static)?
- Why / how are capacitors and inductors dynamic?

5

Capacitor & Inductor Concepts

- Capacitors and inductors store energy
 - Matter that is capable of storing electromagnetic energy is said to have *capacitance* and/or *inductance*
- Energy cannot be stored or extracted instantaneously, but instead requires time
 - Capacitors store electric energy ->
 - Inductors store magnetic energy ->
- Ideal elements: assume internal $R = 0$
- Real elements have (significant) resistance


C & L Properties

- How is energy stored in a capacitor?
- To dc sources, capacitors are seen as _____ circuits (open/short)?
 - dc _____ (current/voltage) is zero?
- How is energy stored in an inductor?
- To dc sources, inductors are seen as _____ circuits (open/short)?
 - dc _____ (current/voltage) is zero?

7


Circuit Analysis with Energy Storage

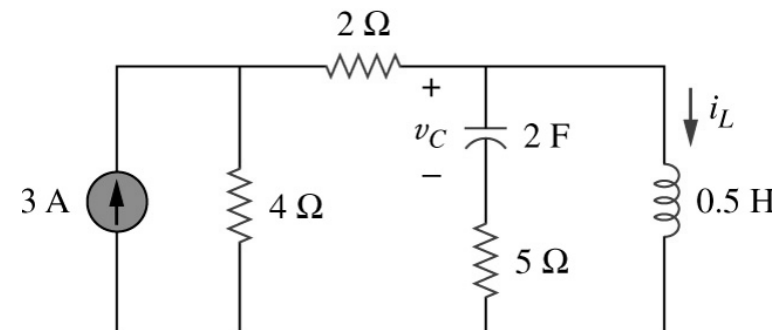- How do we find v_C , i_L and the energy stored in the capacitor and inductor.




Circuit Analysis with an ac Source

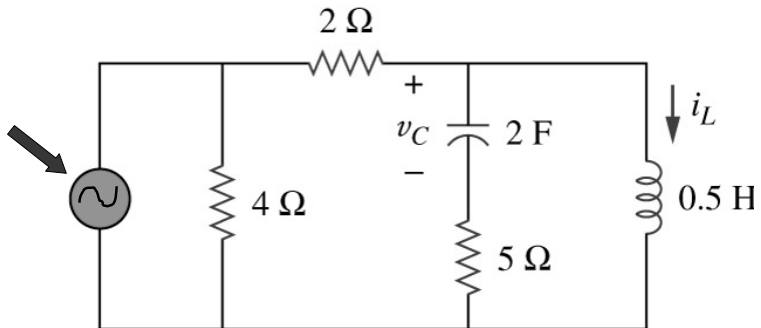- How do we find v_C , i_L and the energy stored in the capacitor and inductor.




ac Waveform

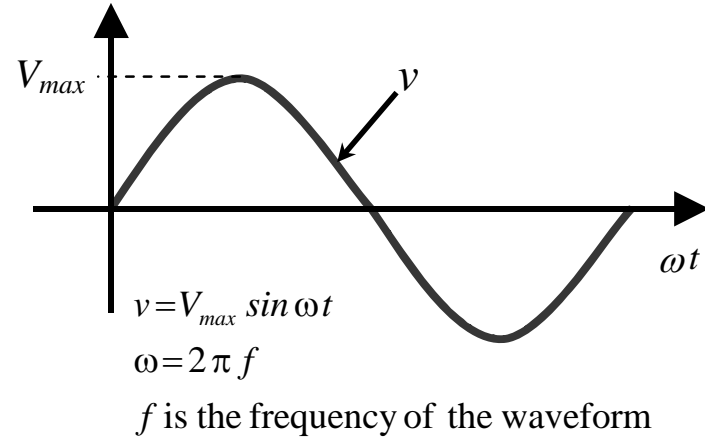

10

AC Phasor Representation

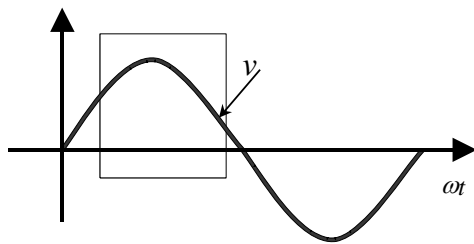


$$V_{rms} = V = \frac{V_{max}}{\sqrt{2}}$$

$$v = V_{max} \sin \omega t$$

$$\omega = 2\pi f = 377 \text{ rad/sec}$$


11

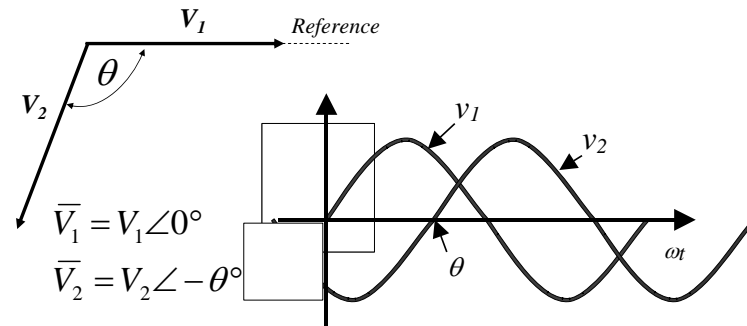

$$v_1 = V_{1max} \sin \omega t$$

$$v_2 = V_{2max} \sin (\omega t - \theta)$$

12

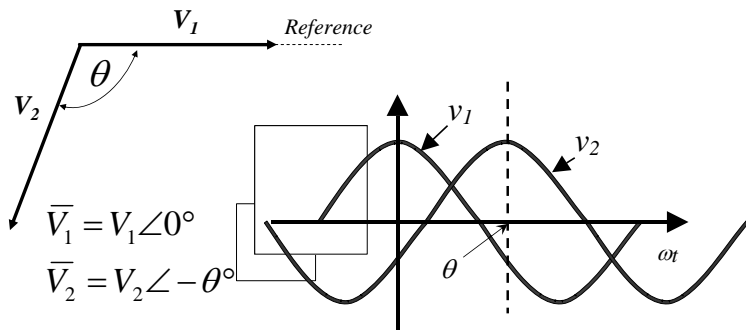


$$v_1 = V_{1\max} \cos \omega t$$

$$v_2 = V_{2\max} \cos (\omega t - \theta)$$

13

Voltage and Current Phase Difference

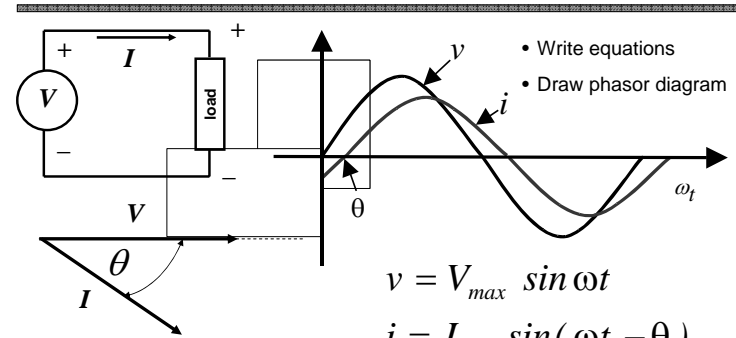

$$\bar{V} = V \angle 0^\circ$$

$$\bar{I} = I \angle -\theta^\circ$$


θ is the phase shift of current
also known as the power factor angle

It is due to the presence of inductive and capacitive elements.

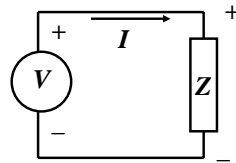Example


If $V=120 \text{ V}$ and $Z=4 + j3 \Omega$,
calculate the current and
power factor.

$$\bar{I} = \frac{\bar{V}}{\bar{Z}} = \frac{120 \angle 0}{4 + j3} = \frac{120 \angle 0}{5 \angle 37^\circ}$$



$$\bar{I} = 24 \angle -37^\circ \text{ A}$$

$$pf = \cos \theta = \cos 37 = 0.8$$

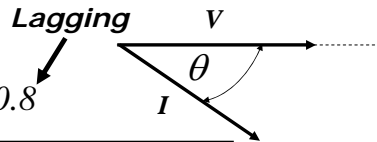


Notice that the *pf angle* is the *angle of the impedance*

15


Application: Phase Shifter

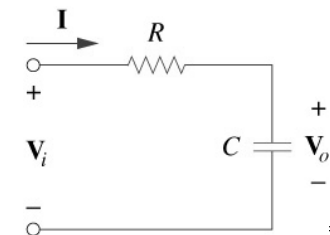- The resistor causes the current to *lead* or *lag* the applied voltage?
- The capacitor causes the current to *lead* or *lag* the applied voltage?




Application: Phase Shifter

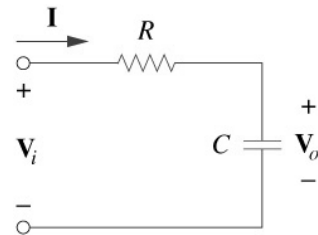- What is the impedance of the circuit?
- How do we find the phase between V_i and I ?
- How do we find the phase between V_i and V_o ?



Application: Voltage Signals

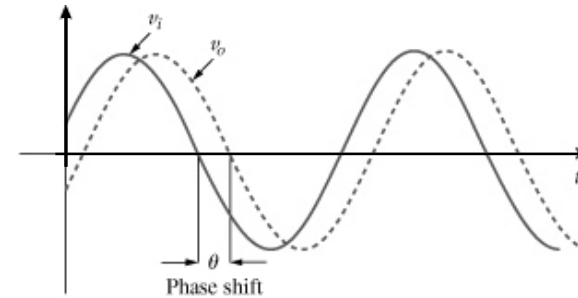- The relative position (phase) of V_i and V_o for the previous circuit.



18

Example: Power Calculations

- The circuit parameters are
 - $V_s = 120\text{V}$ at 60Hz
 - $R_L = 15\Omega$ and $L_L = 0.1\text{H}$
 - $R_{\text{cable}} = 0.5\Omega$ and $L_{\text{cable}} = 0.05\text{H}$
- Find
 - The load impedance
 - The line current
 - The load voltage
 - The complex current
 - The complex load power consumed
 - The complex power lost in the cable
 - The complex power supplied by the source

19

Summary

- AC circuits
 - Sinusoidal steady state
- Energy storage elements
 - Capacitors and inductors
 - Source of phase shift
- Phasors & phase angle
- Complex power
 - Real and reactive power
- Significance of the *power factor*

20